

Name :- Sunnil Dhondumukhade
Roll No:- 36 Class:- TE ENT (A)

Subject:- Power Device And Circuits


College:- Modern Education Society's Wadia
College Of Engineering, Pune

09/01/24

UNIT I: STUDY OF POWER DEVICES


- * SCR (Silicon Controlled Rectifier) (Thyristor)

Construction:-

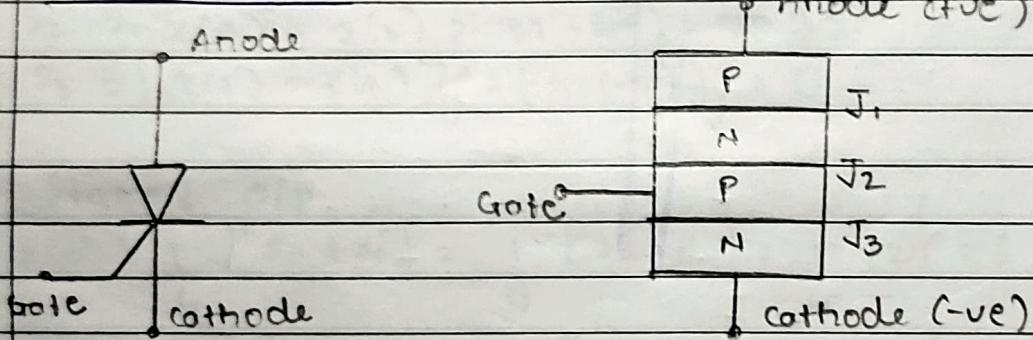

1. Solid state operating devices.
2. It has four layers (P, N, P, N), three junctions (J_1 , J_2 , J_3), three terminals (Anode, Cathode, Gate).
3. It is a current operating device.
4. In off state it has infinite resistance & in ON state it has low resistance (0.01 Ω to 1 Ω)

Two Transistor Model or Analogy

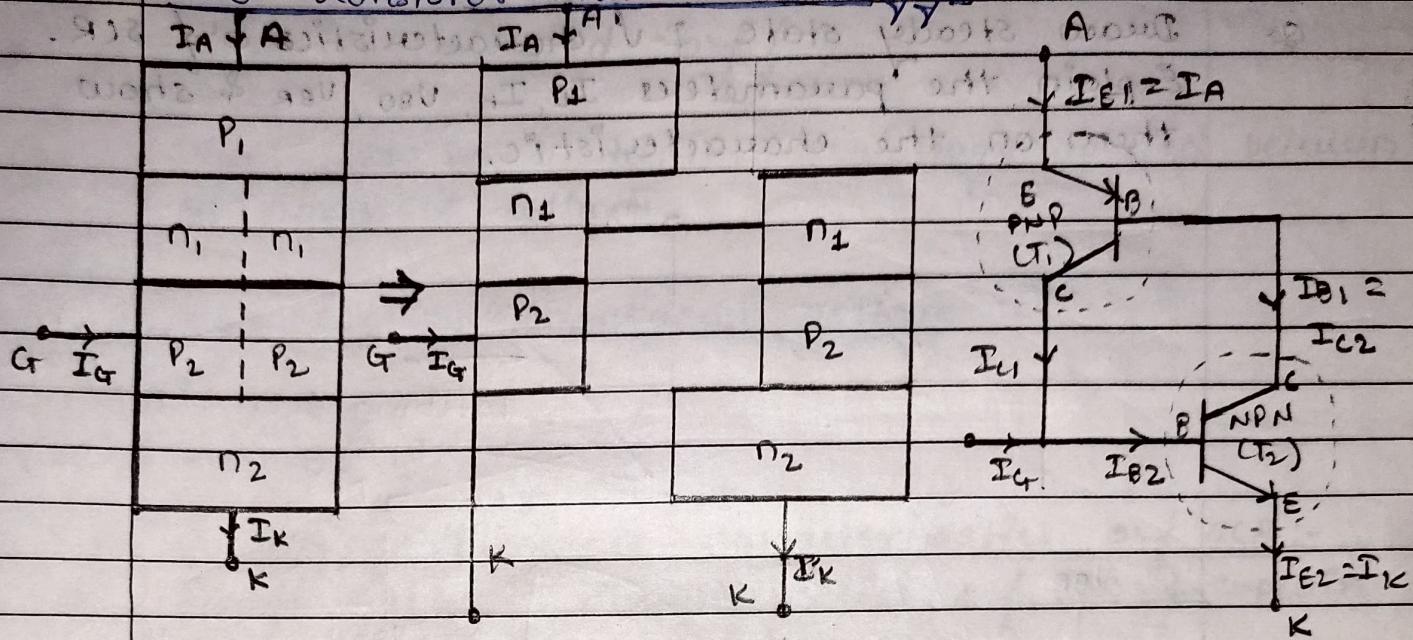

I_G \Rightarrow Gate Current

I_{CBO} \Rightarrow Collector Leakage Current with zero base current



α \Rightarrow DC current gain

Important Features of SCR:-

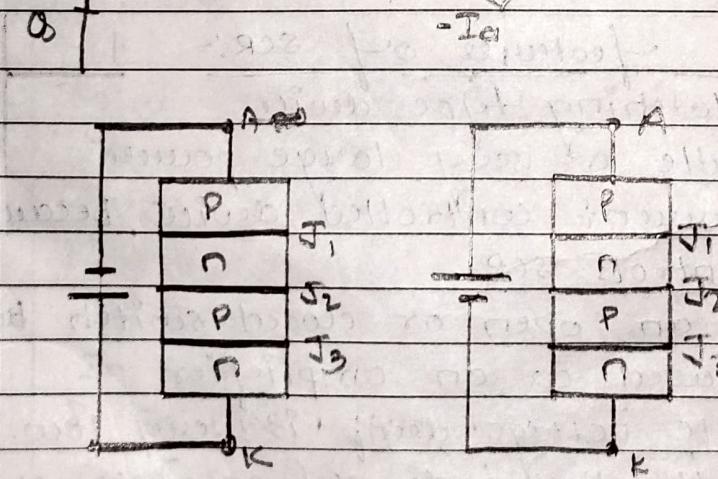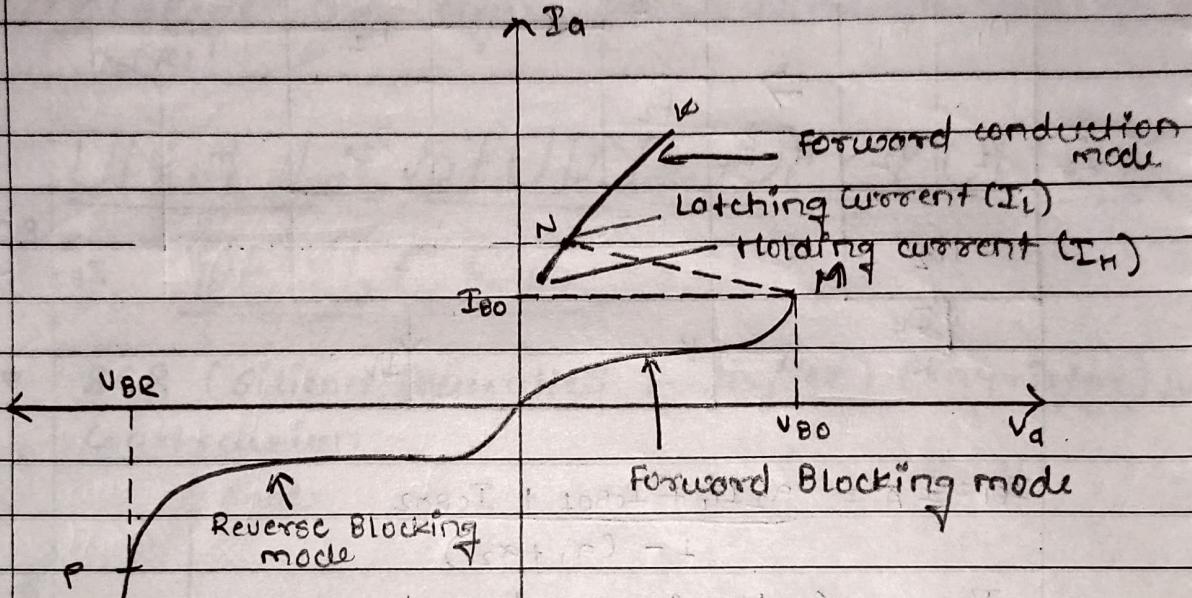1. It is a latching type device.
2. It can handle a very large power.
3. It is a current controlled device, because the gate current controls SCR.
4. It acts as an open or closed switch but it cannot be used as an amplifier.
5. The on-state voltage drop is very low.
6. It can handle thousands of amperes of current.

I-V characteristic of SCR :-

Q:- Draw steady state I-V characteristics of SCR. Explain the parameters I_L , I_H , V_{BO} , V_{BR} & show them on the characteristic.



V_{BO} :-

I_L :- Minimum anode current which SCR must attain during turn-on process to maintain conduction.

$I_L \leftarrow I_{H_1}$:- Minimum anode current below which SCR is turned off.

V_{BO} :- It is a minimum voltage applied between anode & cathode.

V_{BR} & (Reverse breakdown voltage) :-


* Switching / Dynamic characteristics of SCR :-

Q:- Draw dynamic characteristics of SCR & explain turn-on & turn-off process.

OR

Q:- Draw & explain switching characteristics of SCR.

Turn-on characteristic of SCR :-

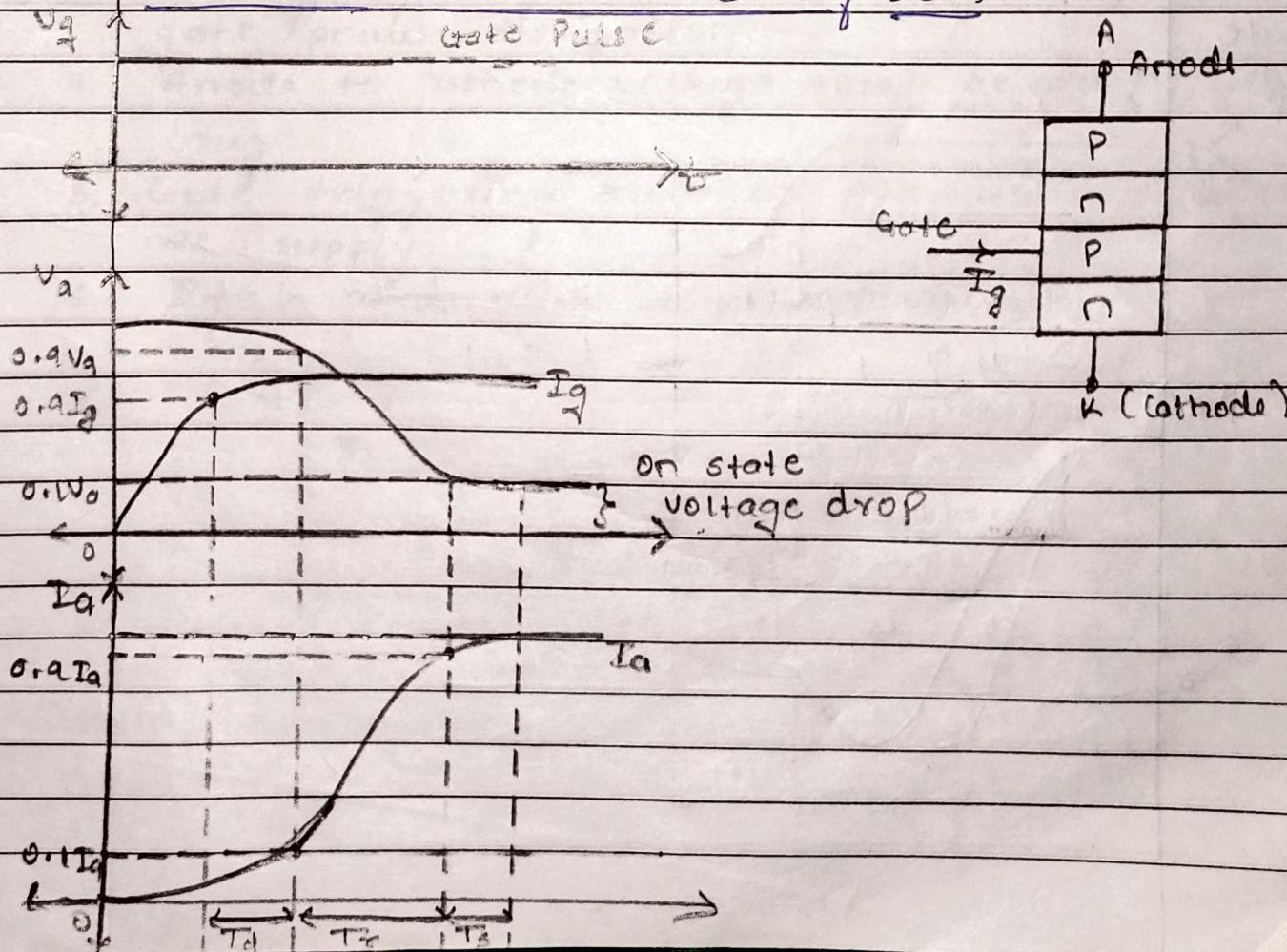

* The Transition time from forward off state to on-state is SCR turn-on time.

T_d :- Gate current reaches 90% of I_g to 20% of I_a . (delay time)

T_r :- Time taken by I_a to rise from 10% to 90% I_a

T_s :- Time taken by I_a to rise from 90% of I_a to final I_a .

Turn-on

$$T_{\text{turn-on}} = T_d + T_r + T_s$$


Two different methods of turning on SCR

Turn off characteristic of SCR :-

Time between ON to OFF state that is, to attain forward blocking mode is turn-off time.

V_a

on state
voltage
drop

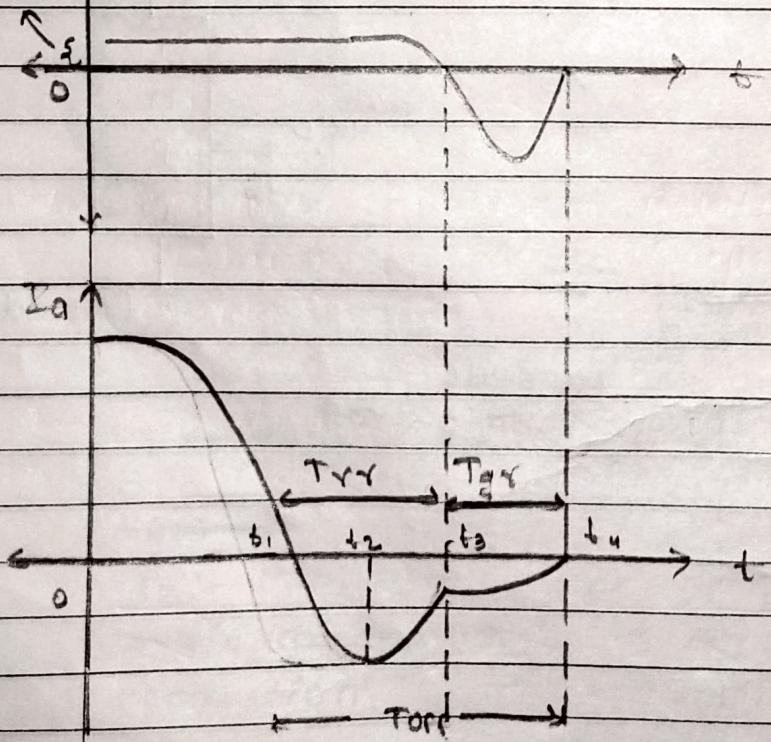


Time (Reverse Recovery time): The time is the time required for the minority carriers to recombine with the opposite charges & get neutralized. It is the time from zero crossover point of SCR current to 25% of the peak reverse recovery current I_{rr} .

T_{gr} : It is the time required for the recombination of excess charges in the middle p-n junction J_2 . A negative reverse voltage will reduce this time.

Necessary conditions

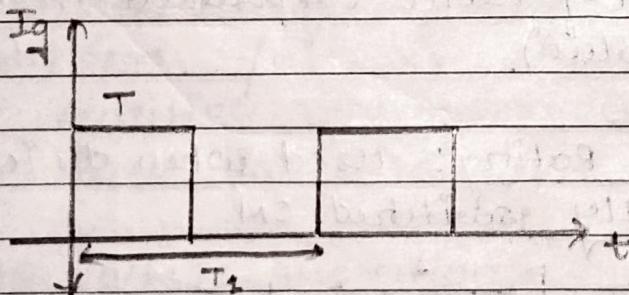- * Necessary conditions for SCR as a switch :-
- 1. SCR must be forward biased.
- 2. $T \geq T_{on}$ of SCR.
- 3. Average gate power dissipation $<$ instantaneous gate power dissipation.
- 4. Anode to cathode voltage must be sufficiently large.
- 5. Gate triggering must be synchronized with AC supply.
- 6. $I_g > \text{min min. required value}$.




101011204

Topic 4:- Thyristor Ratings & Protection:-


* Thyristor Ratings:-

Forward Voltage

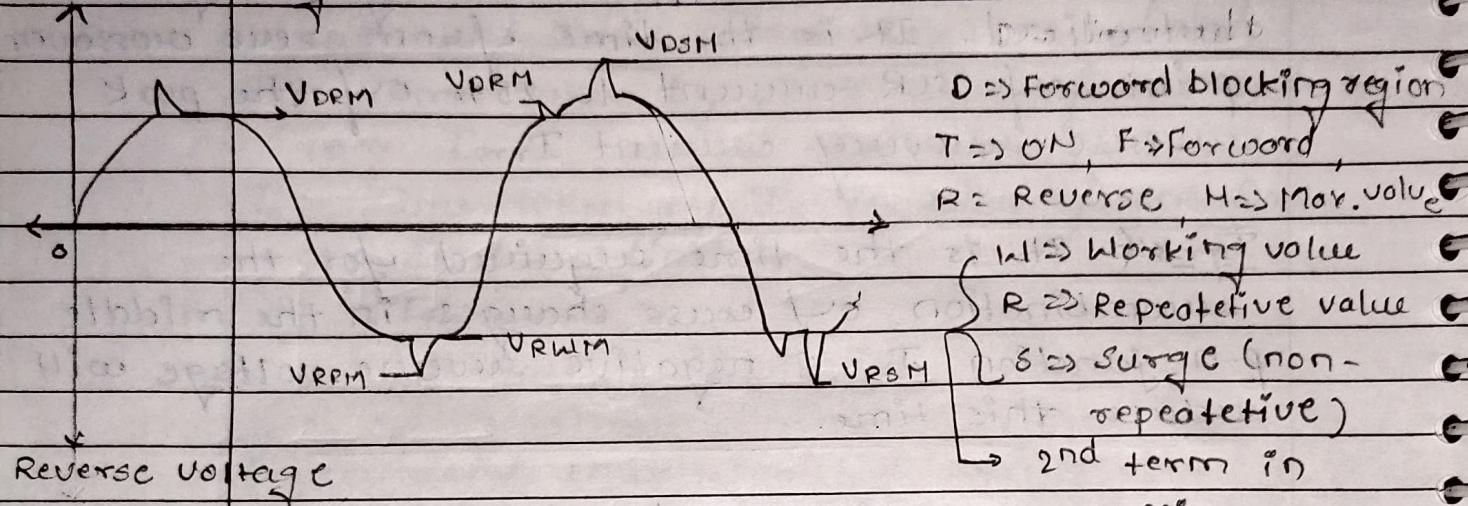

Reverse Voltage

Forward Voltage

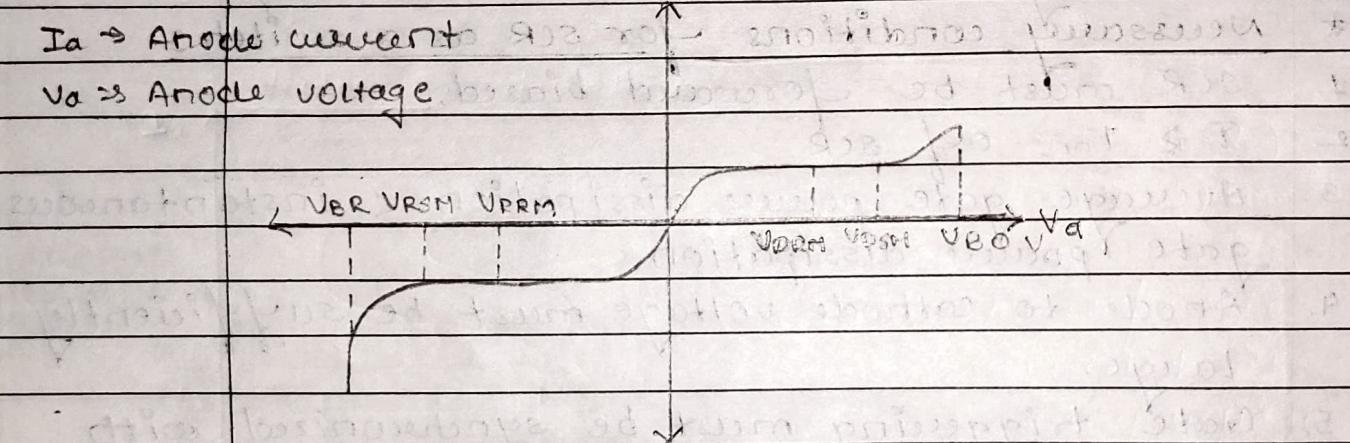

1. Continuous Rating:- Related to continuous working of device (expressed in average or RMS value).

2. Repetitive Rating:- Used when device is periodically switched ON.

3. Surge or Non-repetitive:- Related max. possible current or voltage peaks that the device can withstand during a surge.

\leftarrow see notation

V_{FRM} : It is a peak repetitive forward blocking voltage that a SCR can handle.

V_{RRM} : It is a peak, repetitive reverse voltage that a SCR can withstand.

V_{RWM} : It is a peak working reverse voltage that the SCR can handle.

V_{DSM} : It is a peak surge (non-repetitive) forward blocking voltage. It is less than V_{BO} (Forward Breakover Voltage).

V_{RSM} : It is a peak surge reverse voltage. It is less than V_{BR} (Reverse Breakover Voltage).

* Thyristor Protection:-

If a certain specified limits of thyristor are exceeded beyond its certain limits, then Thyristor Protection is used.

1. Over current protection:-

- i) High Repetitive capacity (HRC) fuse, semi-conductors fuse or rewirable fuse.
- ii) For sensitive systems \Rightarrow Crowbar protection technique is used.


2. Over voltage protection:-

- i) Voltage transients are generated due to different types of switching.
ex:- insulation breakdown, blow of fuse, fuse wheeling diodes, switching of the transformers etc.

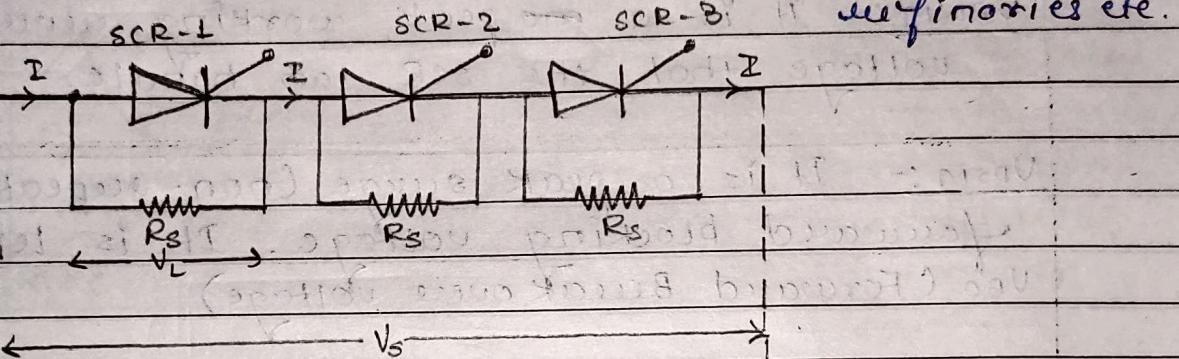
- ii) use low pass filter, zener diodes, snubber circuits etc.

Lecture 5:- Series & Parallel connections of SCRs:-


- * Series connection :- Ex :- Electronic precipitators, surfaceries etc.



Static Equalization :-

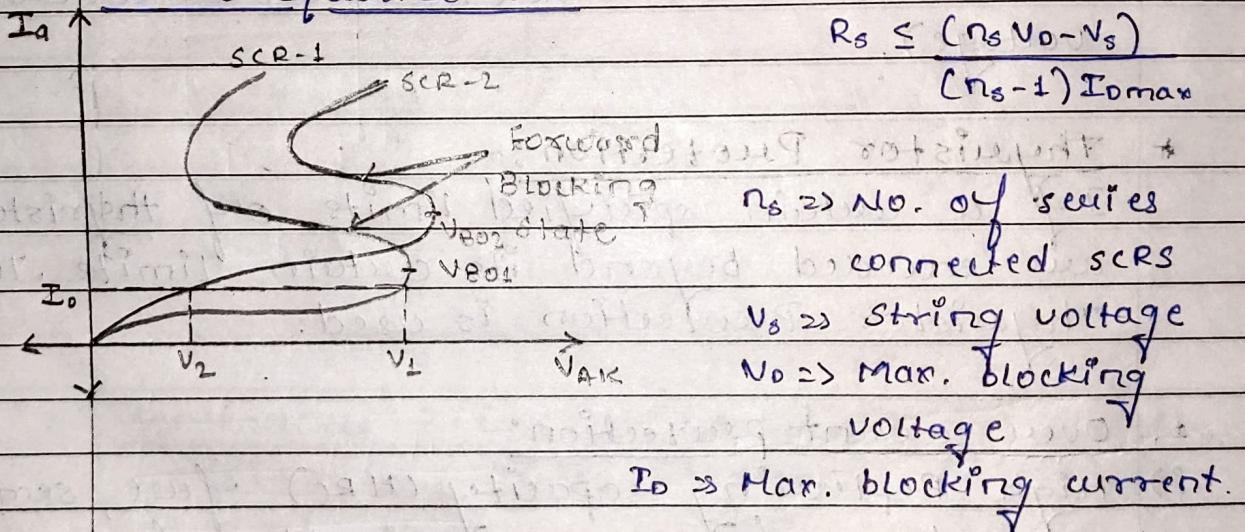

Dynamic Equalization :-

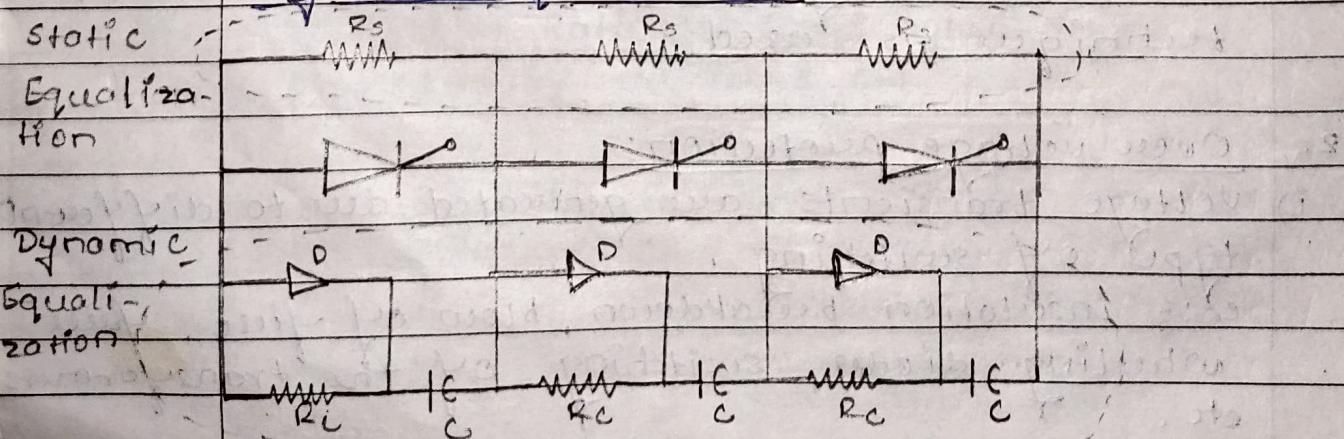

If voltage requirement is more than series connection is preferred by current requirement is more than parallel connection is preferred.


Diode (D) :- i) Make 'C' more efficient in voltage equalization

- ii) Limit $\frac{dV}{dt}$ across SCR.

Advantages:- SCRs of low voltage & high current ratings can be used for serial connection.

Disadvantages:- If equilibration circuit fails then particular SCR may get damaged.

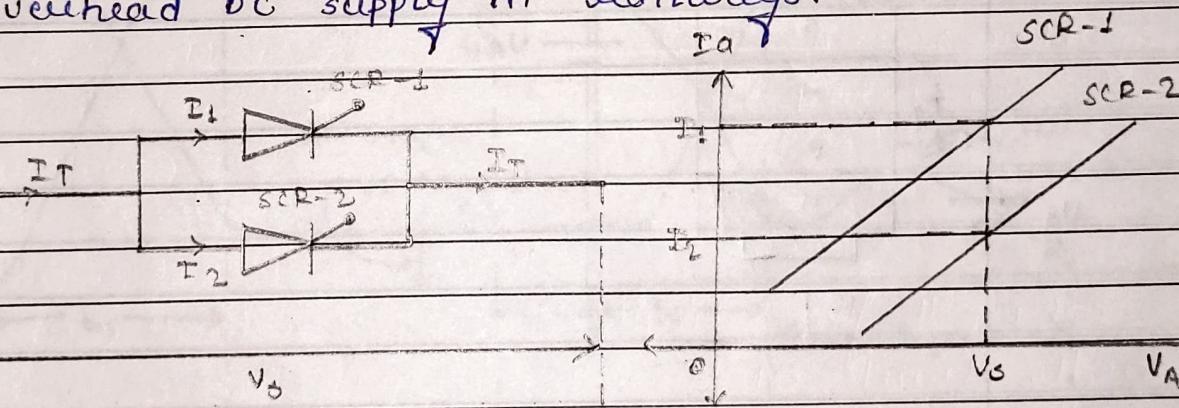
- * Parallel connection:- Ex:- Battery chargers, overhead DC supply in railways.





16101124

Lecture 6:- Gate Turn-off Thyristor (GTO):-

Construction:-

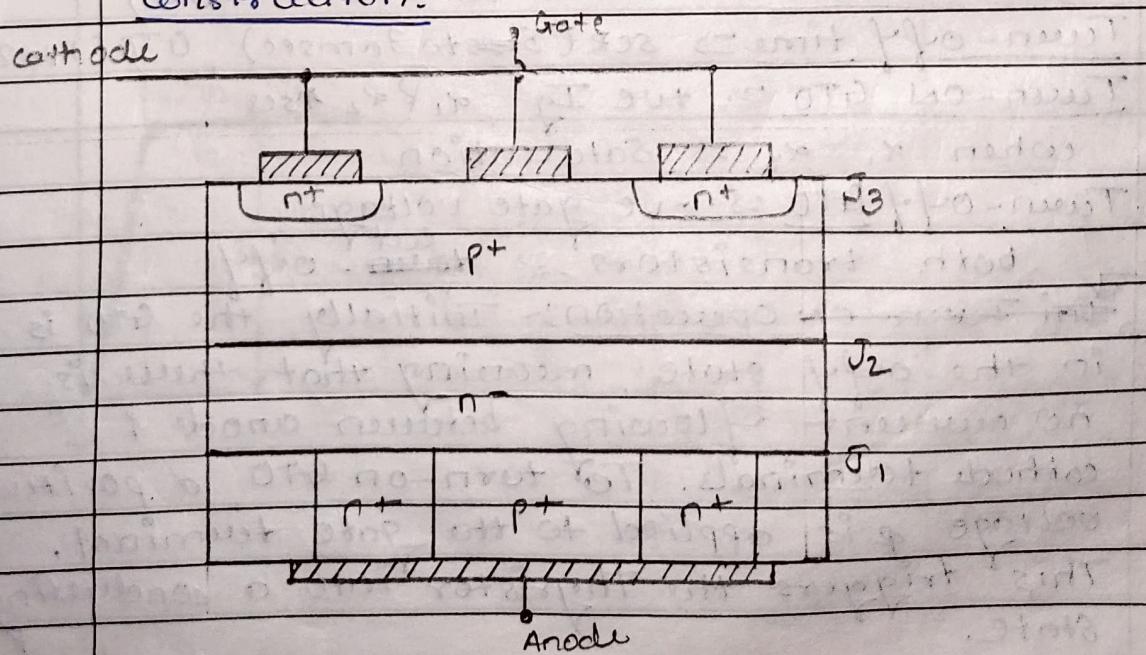

Symbol:-

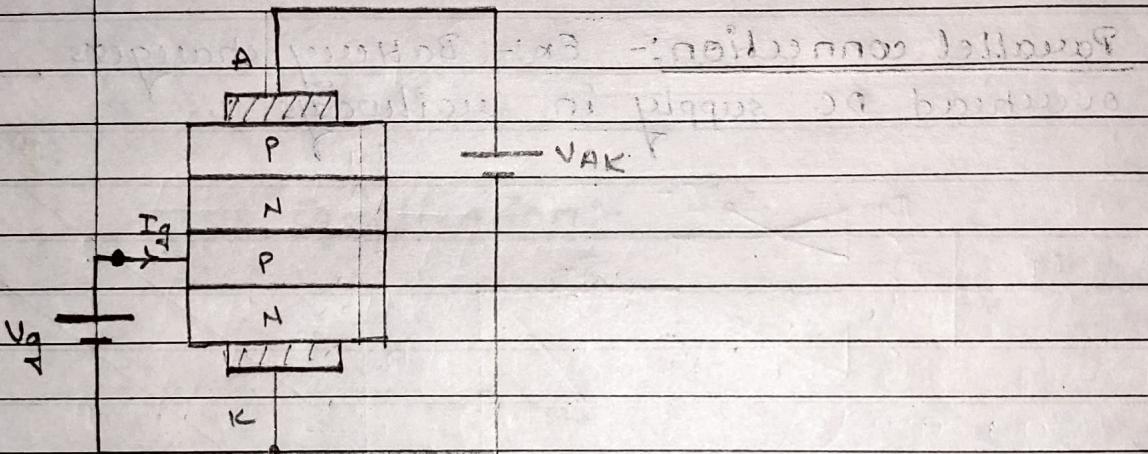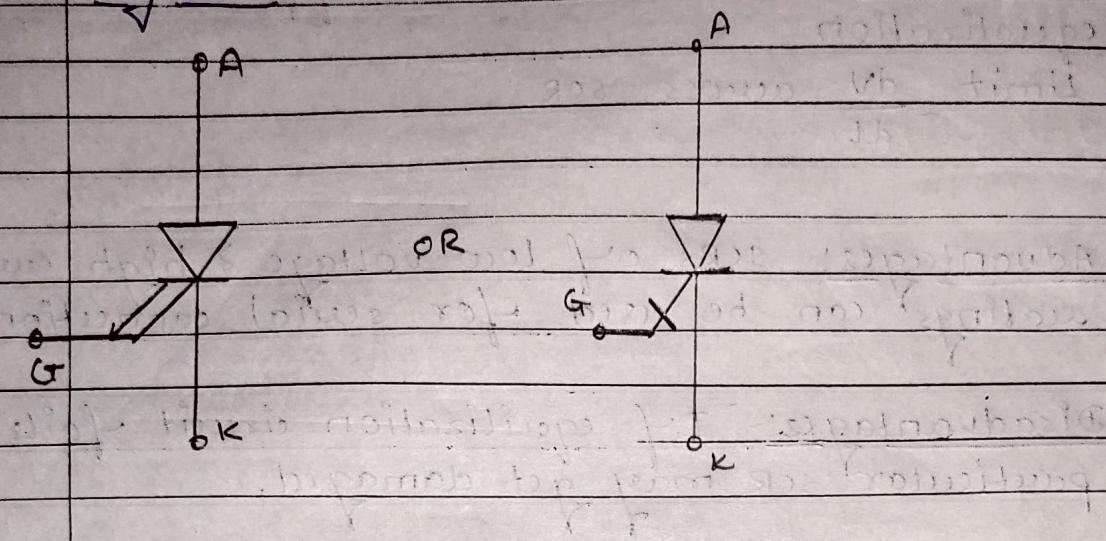

Operation: When a positive voltage is applied to the anode, the GTO turns ON.

Turn-ON time is same as SCR (1ms)

Turn-off time \Rightarrow SCR (5ms to 30ms), GTO ($1\text{to}2\text{ms}$)

Turn-ON GTO \Rightarrow via I_g , $\alpha_1 P \alpha_2$ μs

when $\alpha_1 = \alpha_2 \Rightarrow$ Saturation

Turn-off GTO \Rightarrow -ve gate voltage



both transistors \Rightarrow ~~Cut-off~~ - off

fast explanation \Rightarrow Turn-on operation: Initially, the GTO is in the off state, meaning that there is no current flowing between anode & cathode terminals. To turn-on GTO, a positive voltage V is applied to the gate terminal. This triggers the Thyristor into a conducting state.

Conduction: Once the GTO is turned on, it remains in conduction state.

Turn-off mechanisms: To turn-off the GTO, a negative voltage pulse is applied to the gate terminal. This negative pulse neutralizes the positive charge carriers in the thyristor, reducing the current flow to zero & turning off the device.

Switching characteristics:

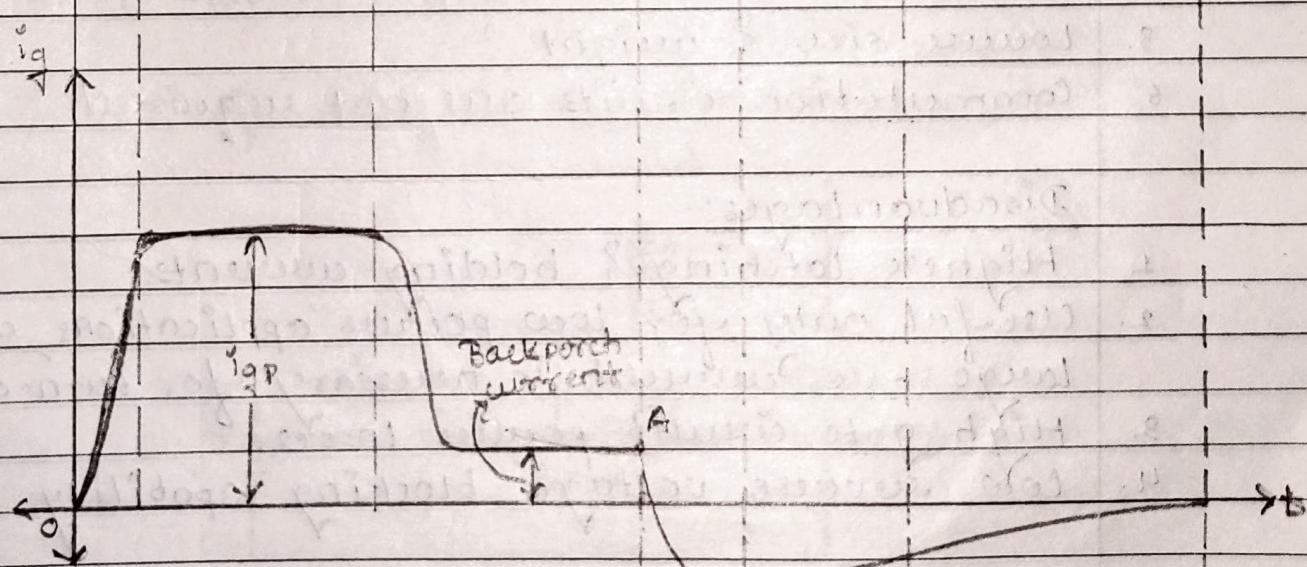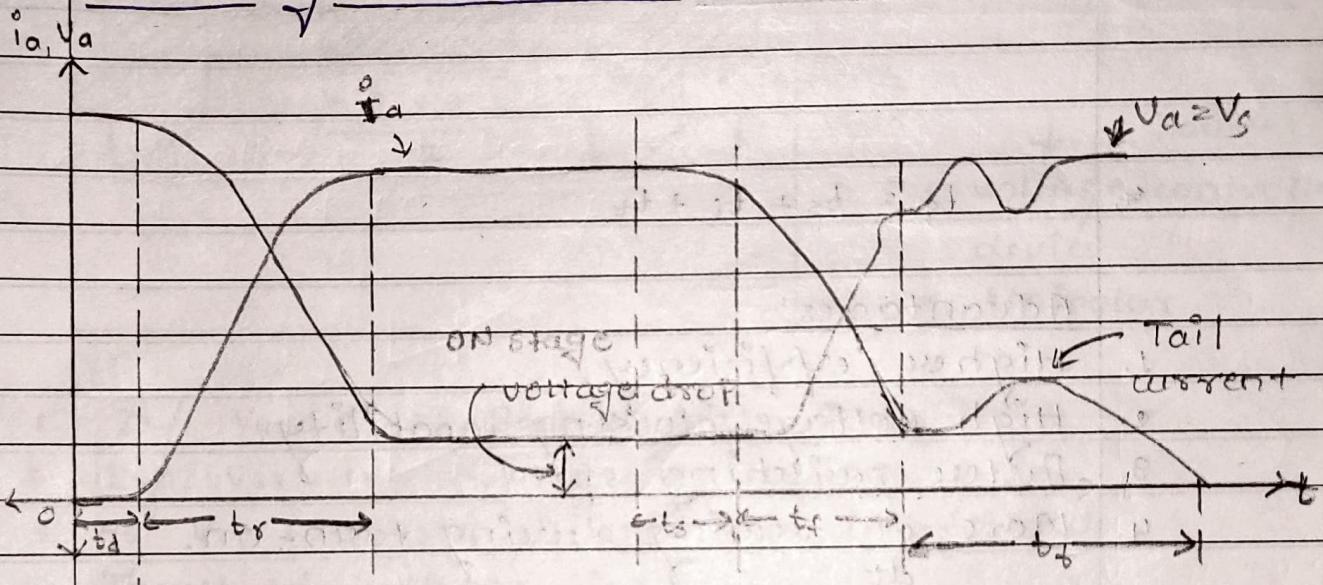

1. Storage time (t_s):- It is the time required to remove excess charge. It is called storage time (t_s).

2. Fall time (t_f):-

3. Tail time (t_t):-

4. $t_g = t_s + t_f + t_t$

Advantages:-

1. Higher efficiency.
2. High voltage blocking capability.
3. Faster switching speed.
4. More di/dt rating during turn-on.
5. Lower size & weight.
6. Commutation circuits are not required.

Disadvantages:-

1. Higher latching & holding currents.
2. Useful only for low power applications, as large -ve current is necessary for turn-off.
3. High gate circuit power losses.
4. Low reverse voltage blocking capability.


Applications:-

1. High performance drive systems ex:
Rolling mills, Robotics, etc.

2. Counters, pulse generators, multi-vibrators.
3. Used for traction purposes.
4. Adjustable frequency inverter drives.


26/01/24 Lecture 7 :- P-channel MOSFET

* n-channel E-MOSFET :-

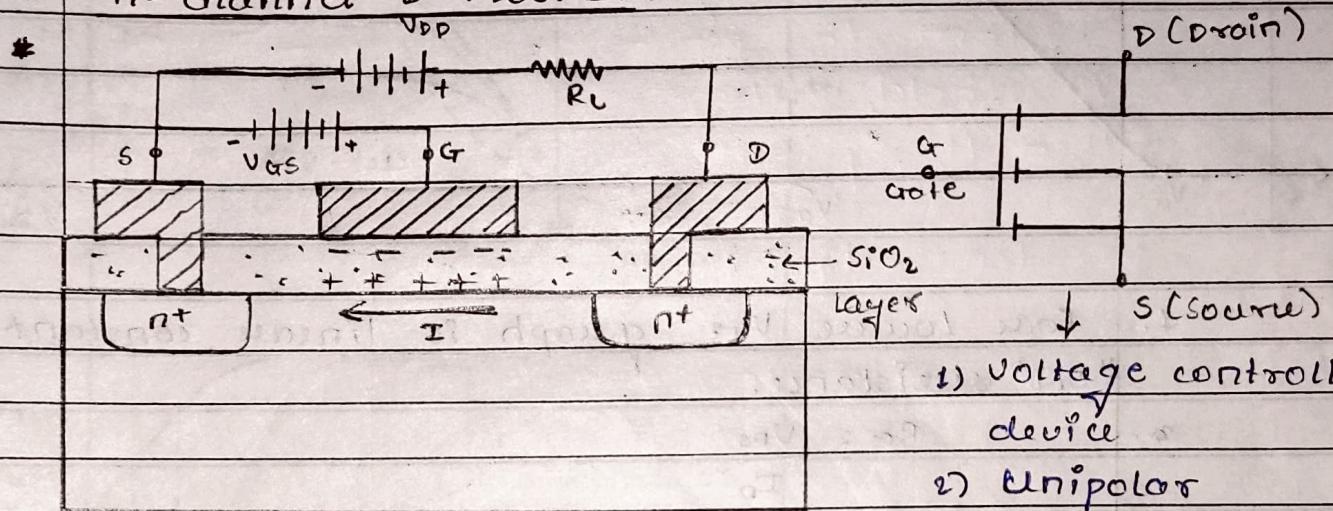


1. If $V_{GS} = 0 \Rightarrow$ Reverse bias, $I = 0$.
2. If $V_{GS} = +ve \Rightarrow$ depletion region.
3. As V_{GS} increases, 'n' channel is formed.
4. Threshold voltage V_{GST} .

Steady-state characteristics :-

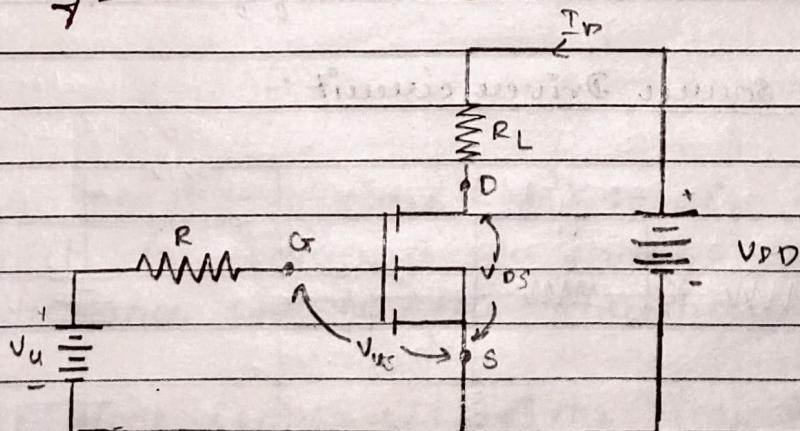

Transfer characteristic :-

Output characteristics

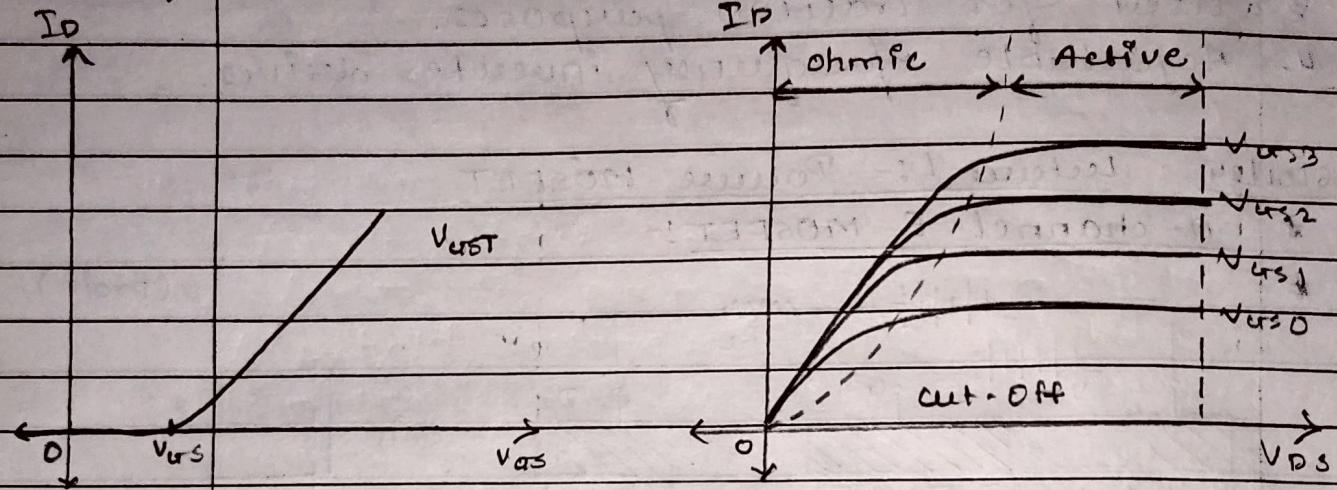


- For low V_{DS} , graph is linear, constant "ON" resistance.
 - $R_{DS} = \frac{V_{DS}}{I_D}$
 - For given V_{DS} , if I_D is const., O/p is flat ($I_D = \text{const.}$)
 - When derived with large V_{DS} , PMOSFET is "ON".

$V_{DS(\text{const})}$ is small \Rightarrow closed switch in ohmic region.


 - When $V_{DS} < V_{GS(\text{off})} \Rightarrow$ cut-off \Rightarrow open switch.

Gate - Source Drive circuit :-

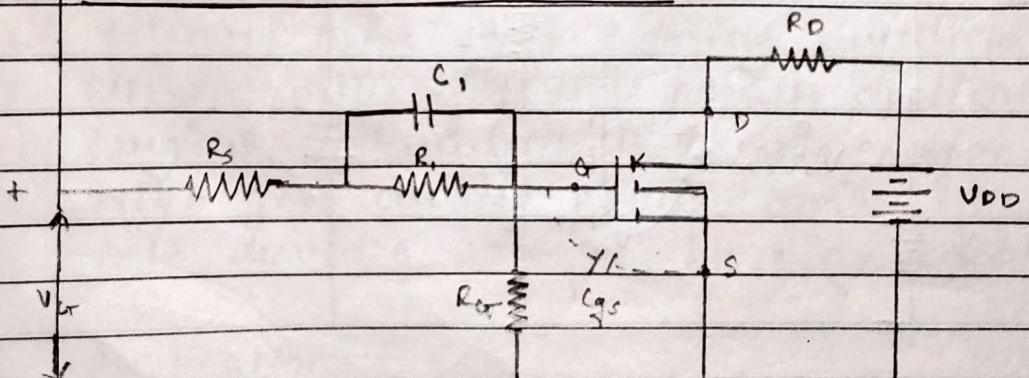

$$I_{CRSS} = \frac{V_G}{R_s + R_i + R_{OT}} \Rightarrow V_{CRS} = \left(\frac{V_G}{R_s + R_i + R_{OT}} \right) R_{CR}$$

Switching characteristics :-

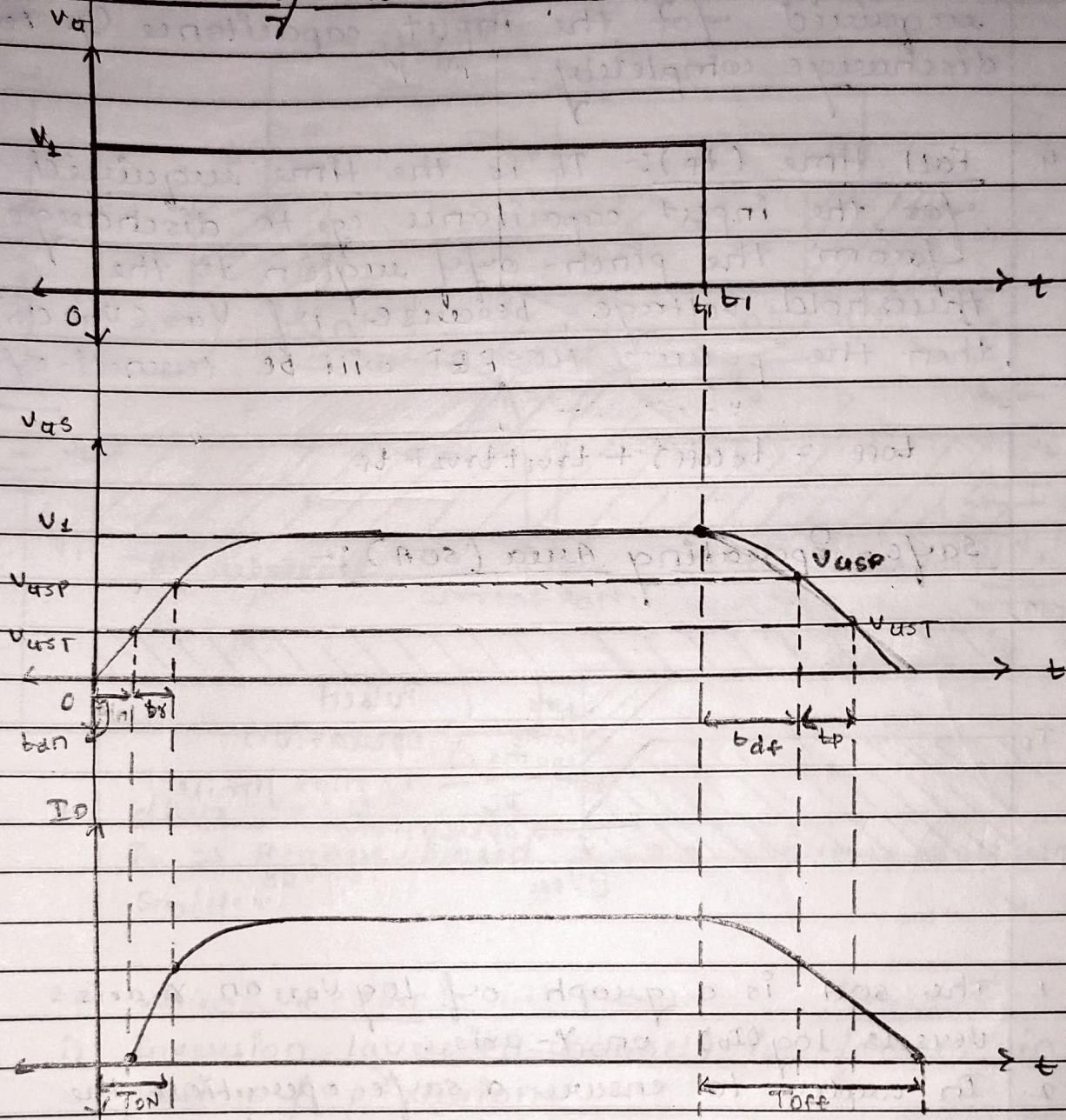


1. Turn on delay time (t_{ON}) :- It is the time which is required to charge the input capacitance (C_{gs}) to the threshold voltage ($V_{gs(th)}$).
2. Rise time (t_R) :- It is the time taken by V_{ds} to rise from the threshold voltage ($V_{ds(th)}$) to the full gate voltage (V_{gs}).

3. Turn-off delay time (t_{doff}):- It is the time required for the input capacitance C_{GS} to discharge completely.

4. Fall time (t_f):- It is the time required for the input capacitance C_{GS} to discharge from the pinch-off region to the threshold voltage, because if $V_{DS} \leq V_{DS(TH)}$, then the power MOSFET will be turned-off.

$$t_{OFF} = t_{dOFF} + t_{RI} + t_{RU} + t_f$$


Safe Operating Area (SOA) :-

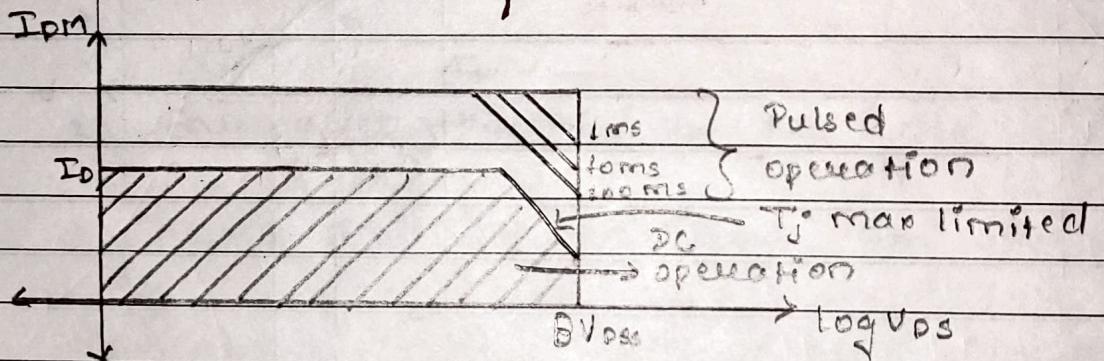

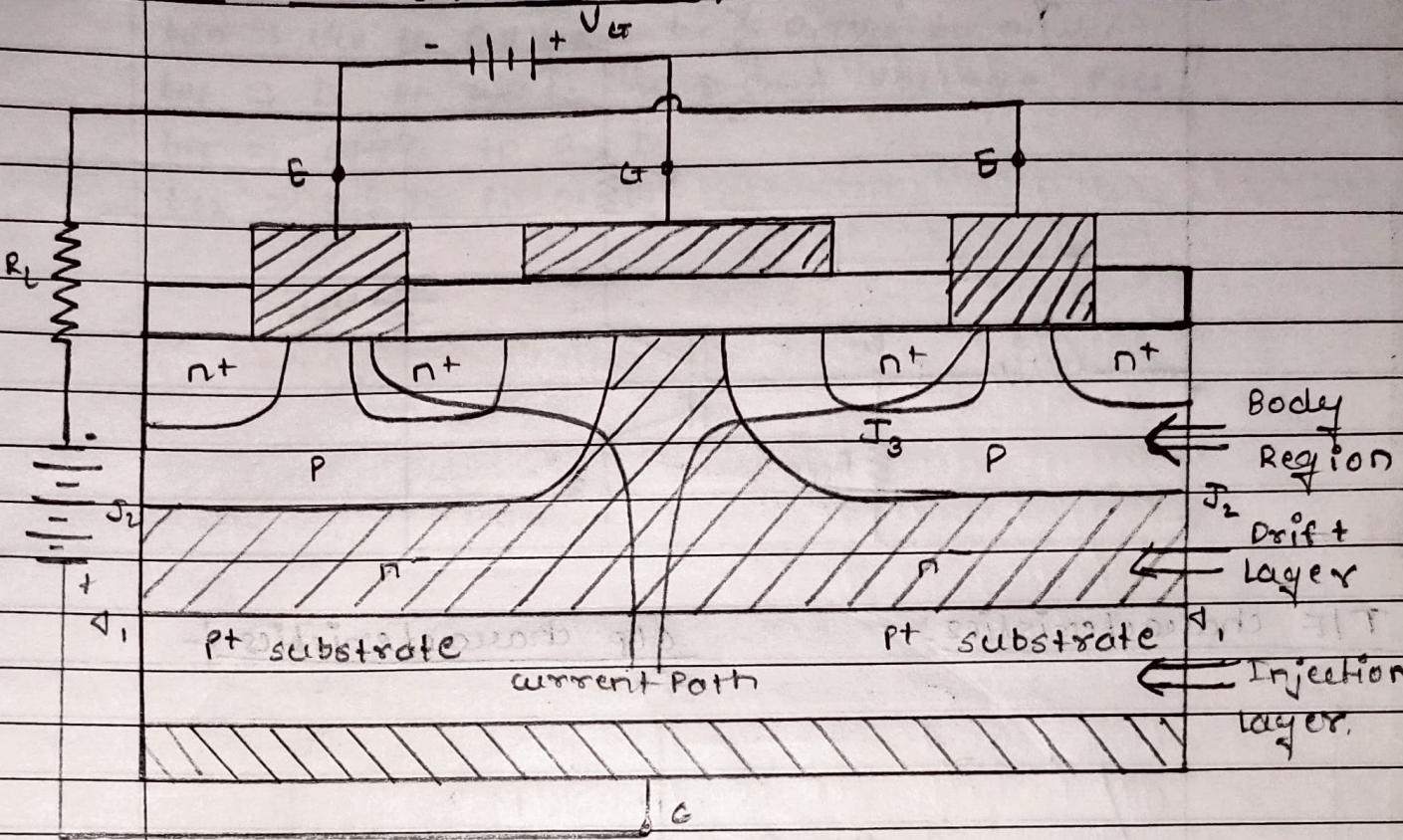1. The SOA is a graph of $\log V_{DS}$ on x-axis versus $\log (I_D)$ on y-axis.
2. In order to ensure a safe operation the device should not operate out of the SOA.
3. Three factors determine the SOA, i.e.
 - i) I_{DM} (Max. drain current).
 - ii) T_j (Junction temperature).
 - iii) BV_{DSS} (Breakdown voltage).

Power MOSFET diagram do from sine notes.

Lecture 8:- Insulated Gate Bipolar Transistor (IGBT) :-




1. When $V_{CE} = 0$:-

$J_2 \Rightarrow$ Reverse biased & $I = 0$ from collector to Emitter.


2. When $V_{CE} > V_{BE}$:-

- i) Inversion layer (n-channel) is formed in upper part of p-region.
- ii) It short circuits n-region & n⁺ emitter region.
- iii) Electrons from n⁺ emitter flows to n-drift region through n-channel.
- iv) Forward biased with 'collector' side & 'emitter' side pt collector injects holes into n-region.
- v) Drift layer is flooded with electrons from 'p' body region & holes from pt collector.


Steady-state characteristics :-

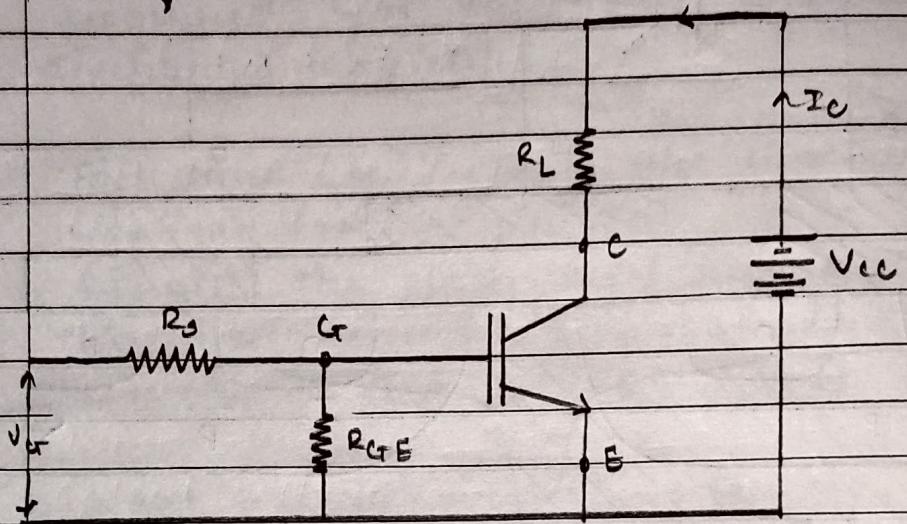


T/F characteristics :-

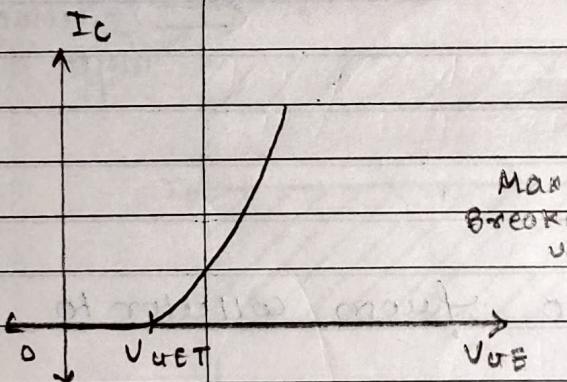

OCP characteristics :-

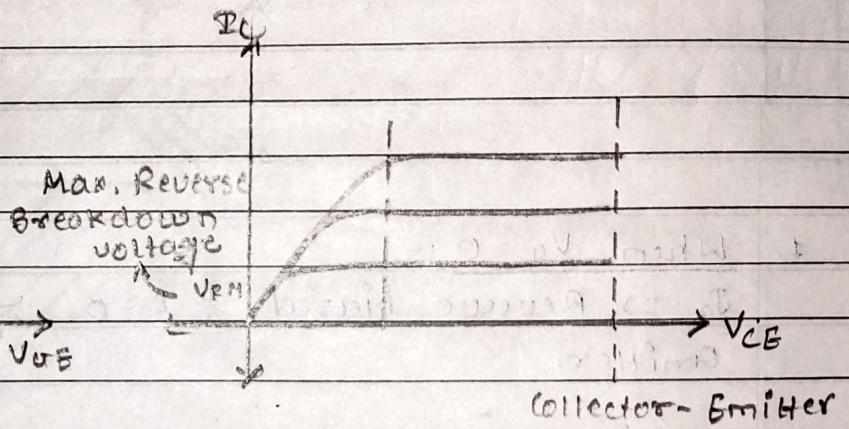

Switching characteristics :-

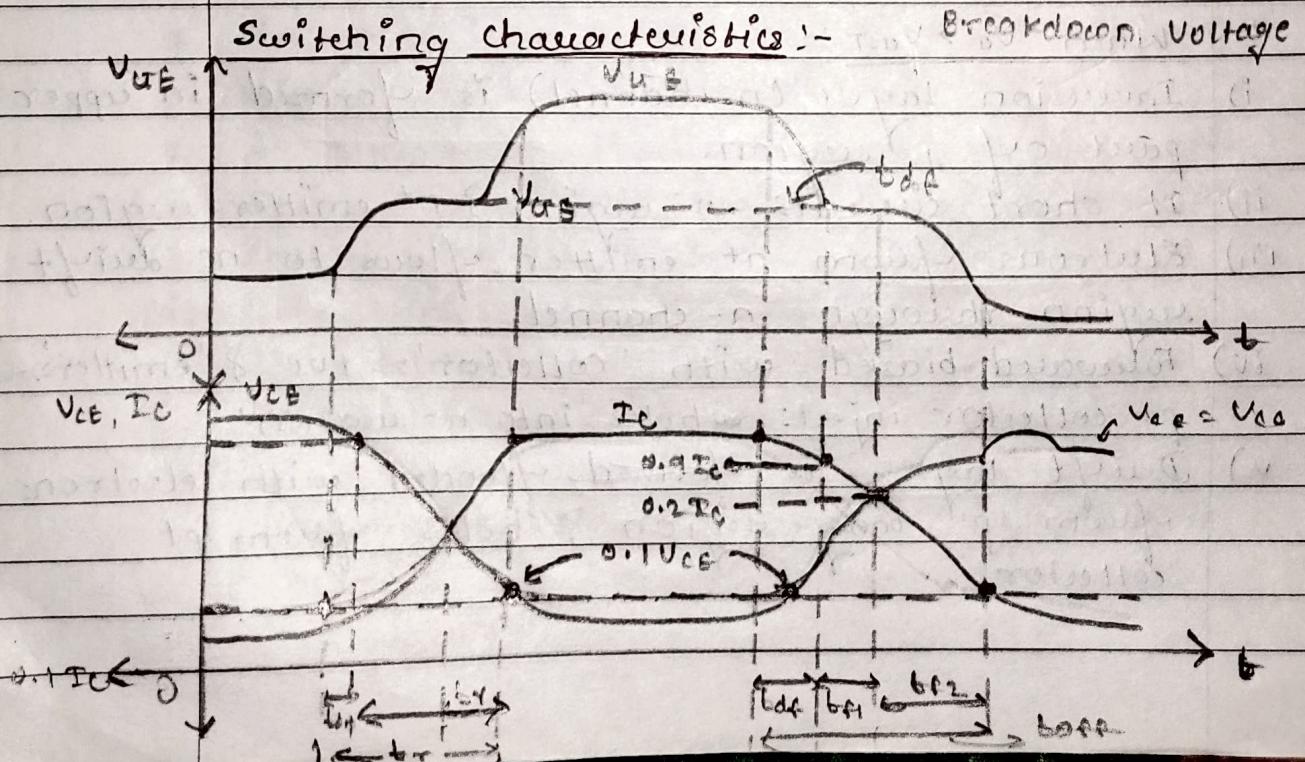

$t_{on} \Rightarrow$ forward blocking to "forward ON" state

$t_{on} \Rightarrow V_{CE} \text{ to } 0.9V_{CE}$, $t_r \Rightarrow 0.9V_{CE} \text{ to } 0.1V_{CE}$

$t_{off} \Rightarrow I_C \text{ to } 0.9I_C \Rightarrow E-C-E \text{ voltage } 1V_{CE}$

$t_{off} \Rightarrow 0.9I_C \text{ to } 0.2I_C$

$t_{off} \Rightarrow 0.2I_C \text{ to } 0.1I_C$

26/01/24

UNIT 2: AC TO DC POWER

CONVERTERS


QUESTION :- Single Phase Half wave controlled rectifier (with R-Load) :-

Q:- What is Phase controlled rectifier (PCR)?


→ Diode Rectifier is uncontrolled
When diode is switched by Thyristor \Rightarrow PCR.
Output voltage can be controlled by changing
firing angle (α)
To turn-on SCR \Rightarrow 1. It must be F.B.

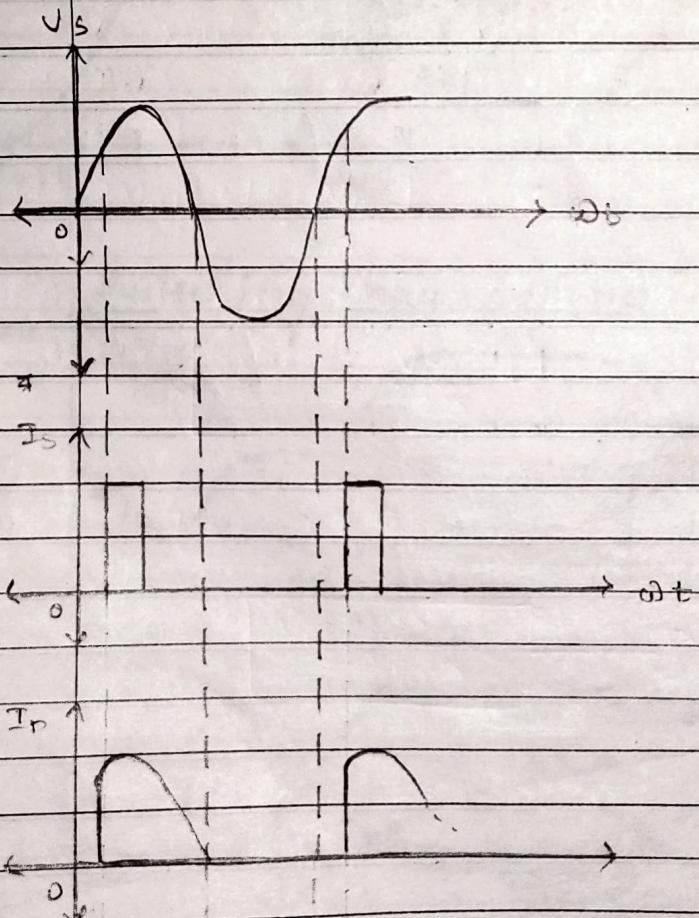2) Gate signal should be applied.

Firing angle (α) is the phase angle of voltage
at which SCR is turned on.



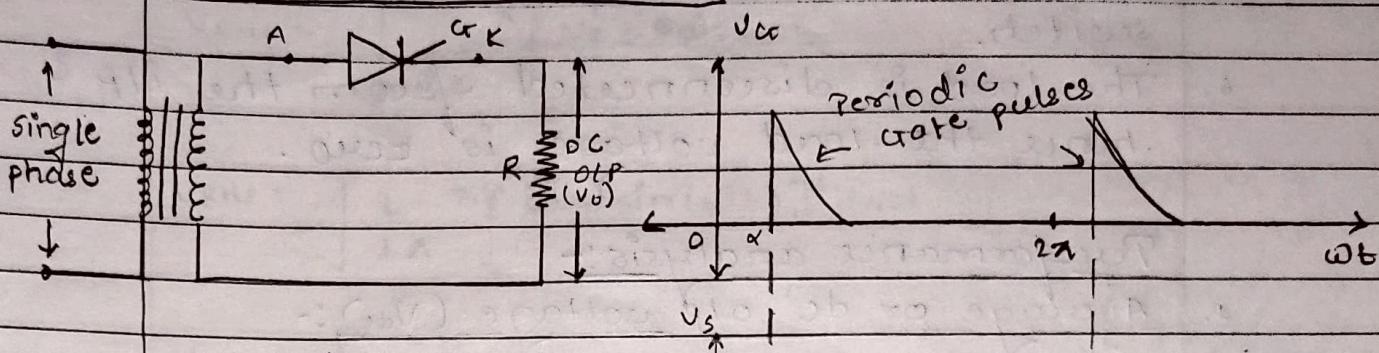* Single Phase Half Wave Controlled Rectifier (HWCR) with R-Load:-



Operation :-

- When it is turned

on at $\omega t = \alpha$

the thyristor acts
like a closed switch

& the input ac

voltage appears

as it is across

the load.

- Due to the

resistive load, the

load current is

in phase with the

load voltage & it

has the same shape,

as that of the

load voltage waveform.

- The instantaneous value of load current is in phase with the load voltage & it has the same shape as that of the load voltage waveform.

- As the load voltage rises, the I_L also rises & as this current reduces below the holding current of SCR, it is commutated due to natural commutation (at $\omega = \pi$).

5. In the negative half cycle, the thyristor is reverse biased, it acts like an open switch.
6. The load is disconnected from the PIP & hence the load voltage is zero.

Performance analysis:-

1. Average or dc op voltage (V_{dc}) :-

$$V_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_o d\omega t \quad \text{--- (1)}$$

$$\text{but } V_o = V_m \sin(\omega t) \text{ or } V_o = V_m \sin \theta$$

$$\text{let } \omega t = \theta \\ d\omega t = d\theta$$

$$V_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \theta d\theta$$

$$V_{dc} = \frac{V_m}{2\pi} \left[-\cos \theta \right]_{\alpha}^{\pi} = \frac{V_m}{2\pi} \left[-\cos(\pi) + \cos(\alpha) \right]$$

$$V_{dc} = \frac{V_m}{2\pi} [1 + \cos(\alpha)] \quad \text{--- (2)}$$

$$\text{if } \alpha = 0$$

$$\therefore V_{dc} = \frac{V_m}{\pi} \quad \text{--- (3)}$$

directly take limits from 0 to π

2. RMS value of output voltage :-

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} V_o^2 d\omega t}$$

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} [V_m \sin(\omega t)]^2 d\omega t}$$

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2(\omega t) d\omega t} = \frac{V_m}{2\sqrt{\pi}} \int_{\alpha}^{\pi} \sin^2(\omega t) d\omega t$$

$$V_{RMS} = \frac{V_m}{\sqrt{\pi}} \sqrt{\frac{1}{2} \int_{\alpha}^{\pi} [1 - \cos(2\omega t)] d\omega t}$$

$$V_{RMS} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\int_{\alpha}^{\pi} d\omega t - \int_{\alpha}^{\pi} \cos(2\omega t) d\omega t}$$

$$V_{RMS} = \frac{V_m}{2\sqrt{\pi}} \sqrt{(\omega t)_{\alpha}^{\pi} - [\sin(\omega t)]_{\alpha}^{\pi}/2}$$

$$V_{RMS} = \frac{V_m}{2\sqrt{\pi}} \sqrt{(\pi - \alpha) + \sin(2\alpha)/2}$$

* AC input power :- $P_i = \frac{V_{RMS}^2}{R} = \frac{V_m^2}{4\pi R} \left[(\pi - \alpha) + \frac{\sin(2\alpha)}{2} \right]$


* DC input power :- $P_o = \frac{V_{dc}^2}{4R} = \frac{V_m^2}{4\pi^2 R} (1 + \cos\alpha)^2$

* Power factor :- $\eta = \frac{P_o}{P_i} = \frac{(1 + \cos\alpha)^2}{\pi \left[(\pi - \alpha) + \frac{\sin(2\alpha)}{2} \right]}$

$$\eta = \frac{4}{\pi^2} - [\alpha = 0 \text{ Max. P.F}]$$

01/02/24


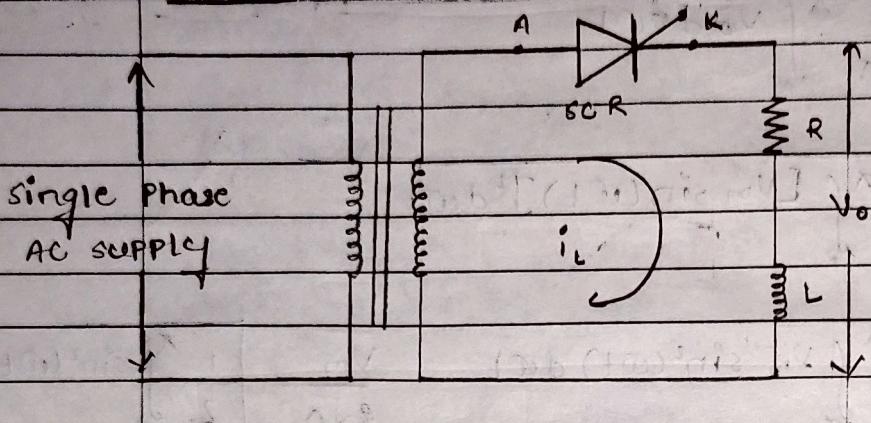
Half Wave Controlled Rectifier with 'R-L' Load :-



Operation :-

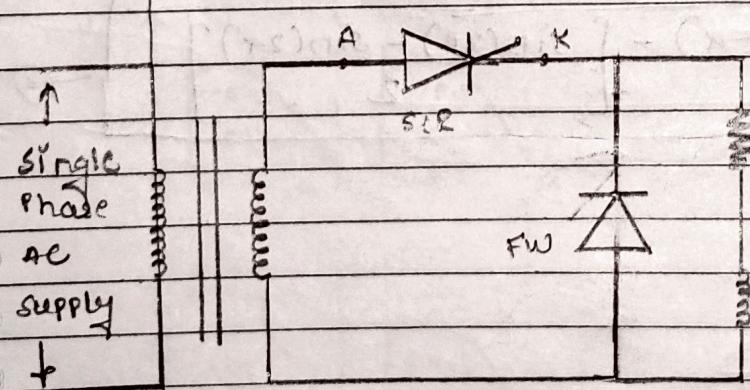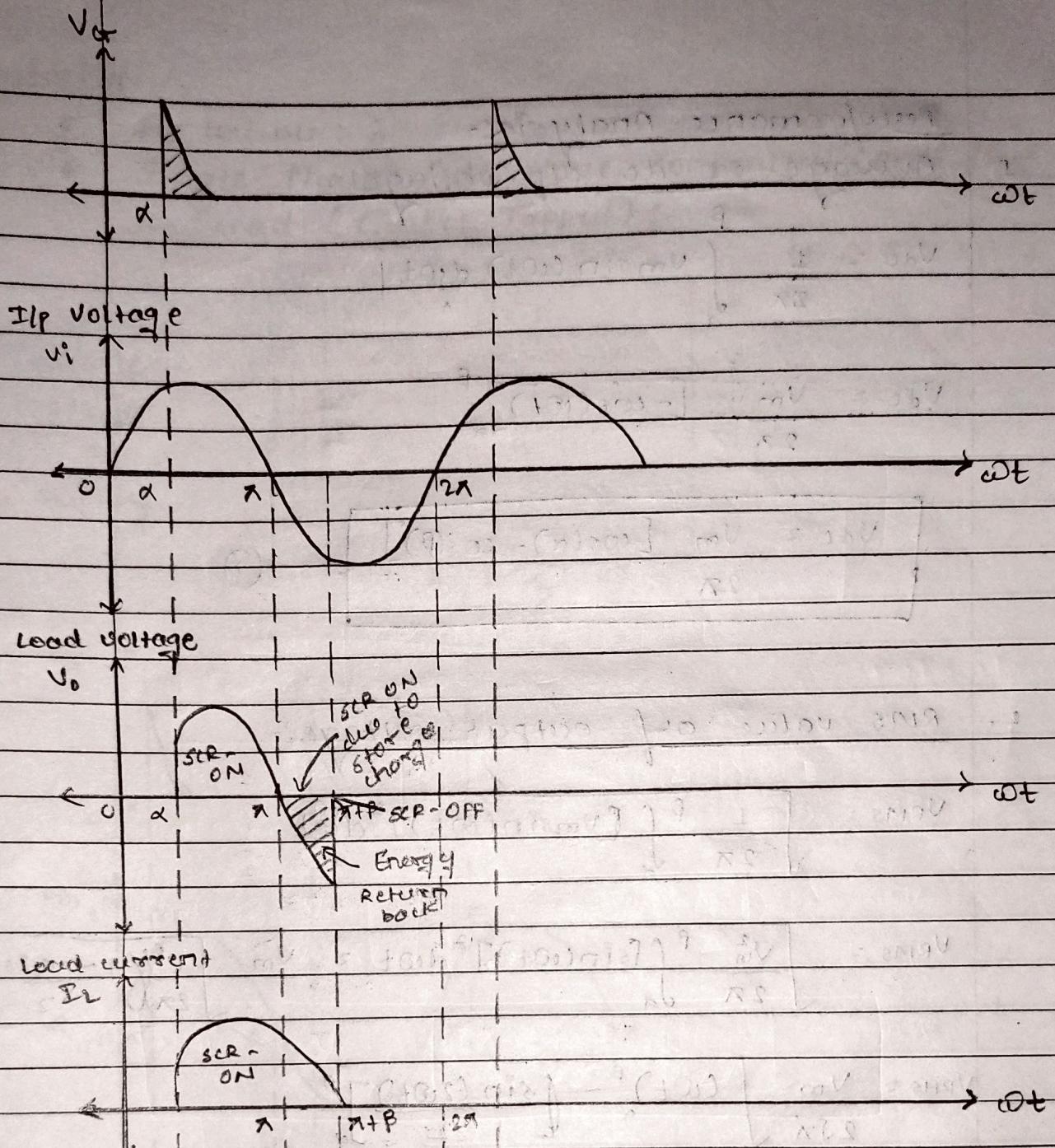1. Mode 1 (0 to α) :- Forward blocking mode
2. Mode 2 (α to π) :- SCR ON, i_L is t.c & increases exponentially
3. Mode 3 (π to β) :- At π , p.v. voltage is zero & after π it becomes -ve. It tries to turn-off SCR, so i_L rises
 - i) But inductive load induces self induced voltage & opposes this change.
 - ii) 'K' voltage becomes more +ve than 'A' voltage.
 - iii) SCR remains in conduction from π to β .
 - iv) Finally I_L becomes 0 at $(\pi + \beta)$ & turns-off SCR.

In the 'R-L' load as energy dissipated through 'R' so that SCR conducts for short-span in the negative half cycle the angle at which SCR stops conducting is called extinction angle (β) where 'I' becomes '0' current remains t.c from α to β .



Free wheeling diode

1. Ilp P.F rises
2. Load current is improved.
3. More olp voltage
4. Efficiency rises
5. conduction time rises.

Performance Analysis:-

1. Average or dc o/p voltage:-

$$V_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin(\omega t) d\omega t$$

$$V_{dc} = \frac{V_m}{2\pi} \left[-\cos(\omega t) \right]_{\alpha}^{\beta}$$

$$\boxed{V_{dc} = \frac{V_m}{2\pi} [\cos(\alpha) - \cos(\beta)]} \quad (1)$$

2. RMS value of output voltage:-

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\beta} [V_m \sin(\omega t)]^2 d\omega t}$$

$$V_{RMS} = \sqrt{\frac{V_m^2}{2\pi} \int_{\alpha}^{\beta} [\sin(\omega t)]^2 d\omega t} = V_m \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\beta} 1 - \cos(2\omega t) d\omega t}$$



$$V_{RMS} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\left[(\omega t) \right]_{\alpha}^{\beta} - \left[\frac{\sin(2\omega t)}{2} \right]_{\alpha}^{\beta}}$$

$$\boxed{V_{RMS} = \frac{V_m}{2\sqrt{\pi}} \sqrt{(\beta - \alpha) - \left[\frac{\sin(2\beta) - \sin(2\alpha)}{2} \right]}} \quad (2)$$

04/02/24

* Lecture :- 3

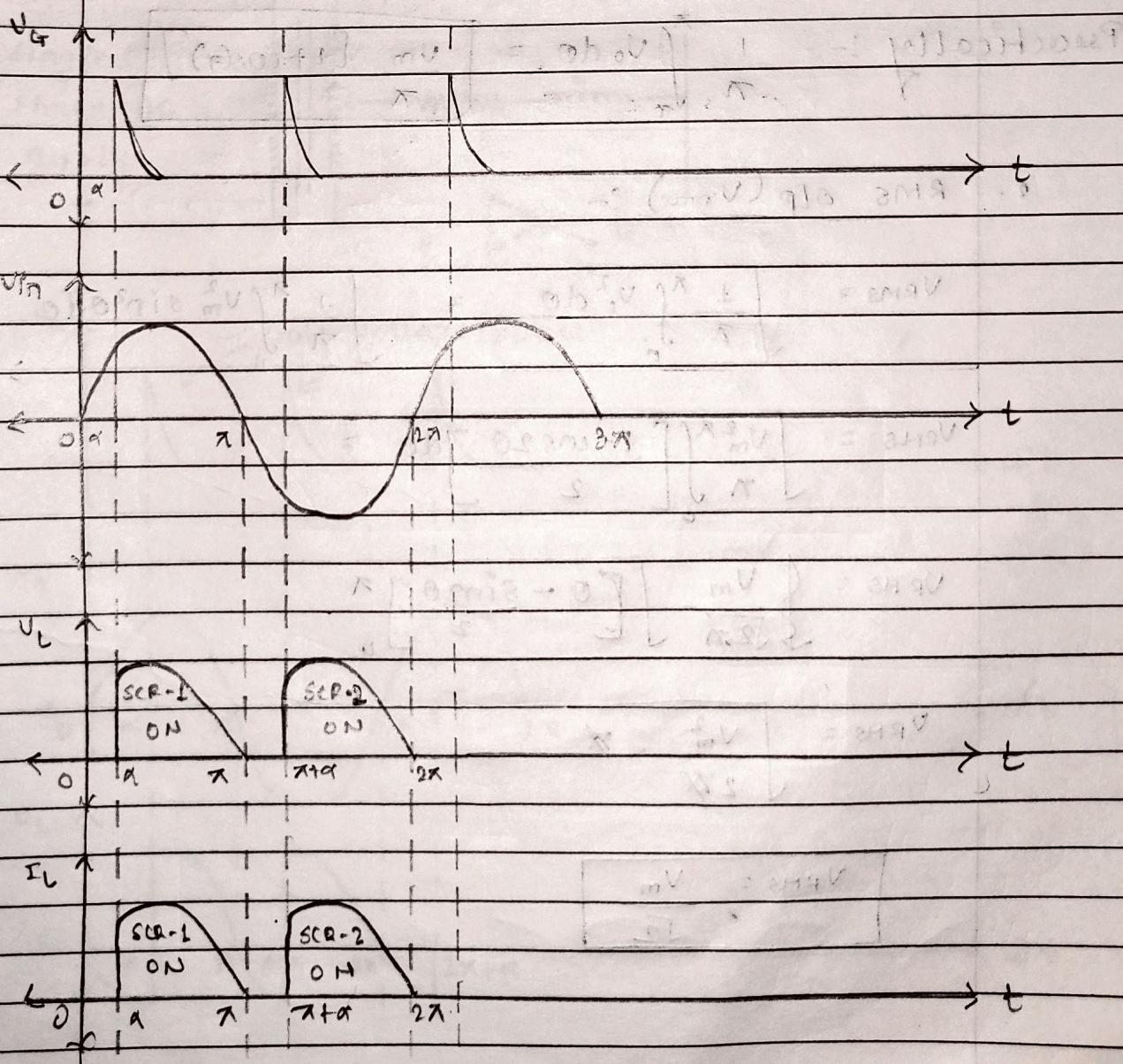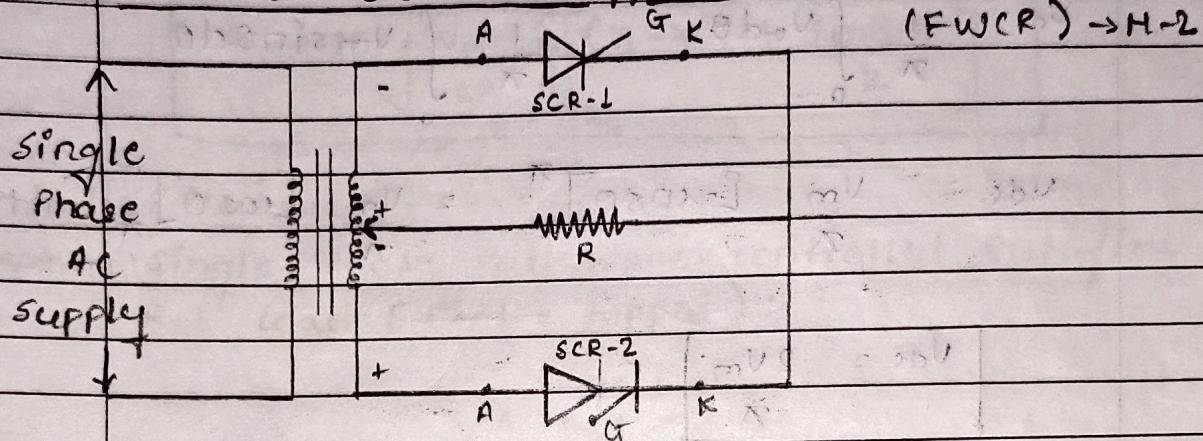* Single Phase Full Wave controlled Rectifier with R-L Load (Centre Tapped) :-



Analysis :-

Average or dc output voltage :-

ideal

$$V_{dc} = \frac{1}{\pi} \int_0^{\pi} V_o d\theta = \frac{1}{\pi} \int_0^{\pi} V_m \sin \theta d\theta$$

$$V_{dc} = \frac{V_m}{\pi} [-\cos \theta]_0^{\pi} = \frac{V_m}{\pi} [\cos 0]$$

$$V_{dc} = \frac{2V_m}{\pi}$$

Practically :- $\frac{1}{\pi} \int_0^{\pi} V_o d\theta = \frac{V_m}{\pi} [1 + \cos \theta]$

2. RMS o/p (V_{rms}) :-

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} V_o^2 d\theta} = \sqrt{\frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2 \theta d\theta}$$

$$V_{rms} = \sqrt{\frac{V_m^2}{\pi} \int_0^{\pi} \left[\frac{1 - \cos 2\theta}{2} \right] d\theta} =$$

$$V_{rms} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\left[\frac{\theta - \sin 2\theta}{2} \right]_0^{\pi}}$$

$$V_{rms} = \sqrt{\frac{V_m^2}{2\pi}} \cdot \cancel{\pi}$$




$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\text{Practically: } V_{\text{RMS}} = \sqrt{\frac{V_m^2}{2\pi} \left[1 - \frac{\sin 2\alpha}{2} \right]^\frac{1}{2}}$$


$$V_{\text{RMS}} = \sqrt{\frac{V_m^2}{2\pi} \left\{ \left[(\pi - \alpha) + \frac{\sin(2\alpha)}{2} \right] \right\}^\frac{1}{2}}$$

07/02/24 Lecture 4:-

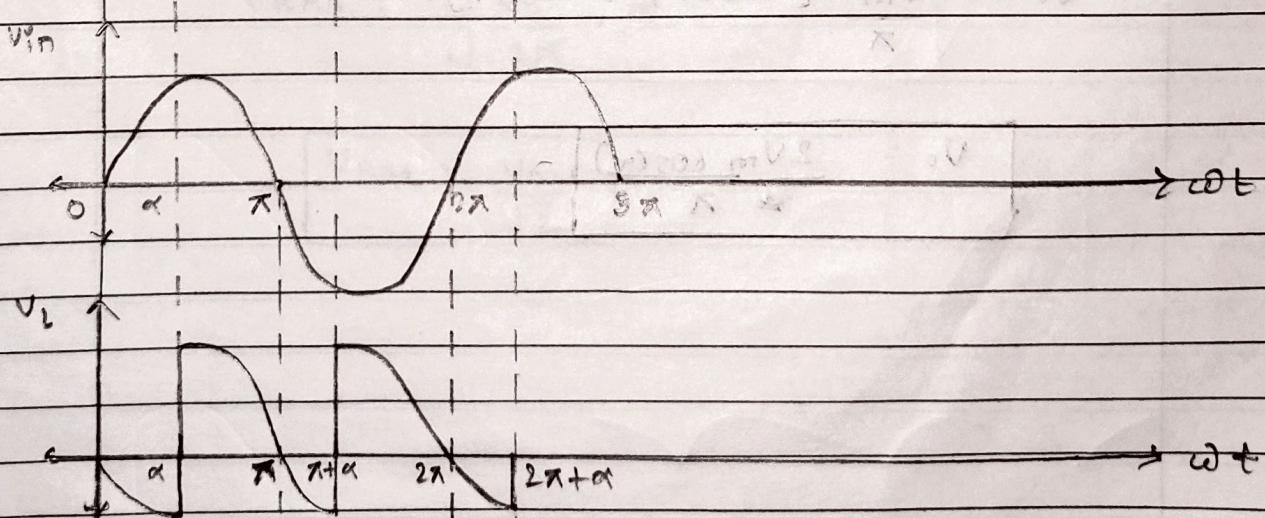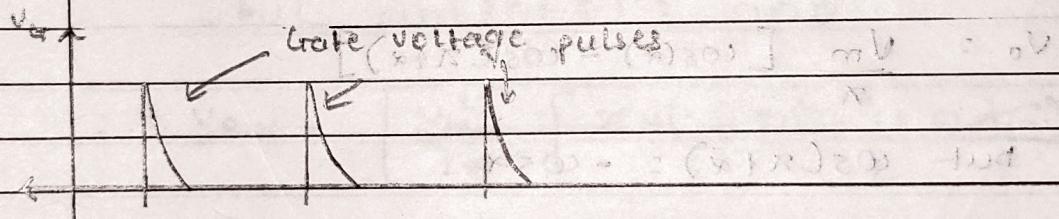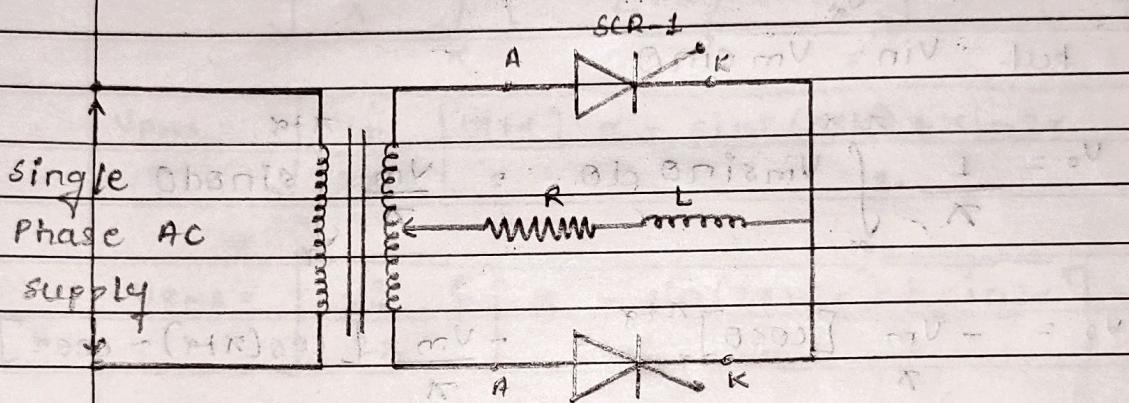~~**~~ single Phase Full Wave-controlled Rectifier with R-L Load (Centre tapped) :-



It is also called M-2 or BWCR

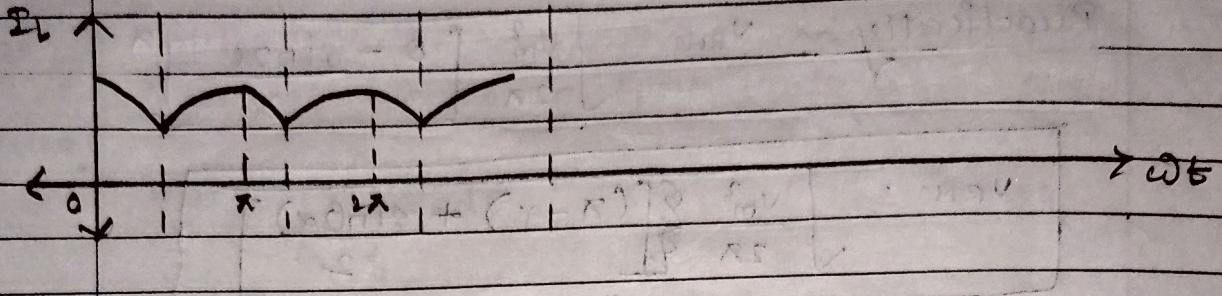

Performance Analysis:-

2. Average O/P voltage :-

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_{in} d\theta$$

$$\text{but } V_{in} = V_m \sin \theta$$

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \theta d\theta = \frac{V_m}{\pi} \int_{\alpha}^{\pi+\alpha} \sin \theta d\theta$$

$$V_o = -\frac{V_m}{\pi} [\cos \theta]_{\alpha}^{\pi+\alpha} = -\frac{V_m}{\pi} [\cos(\pi+\alpha) - \cos \alpha]$$

$$V_o = \frac{V_m}{\pi} [\cos \alpha - \cos(\pi+\alpha)]$$

$$\text{but } \cos(\pi+\alpha) = -\cos \alpha$$

$$V_o = \frac{V_m}{\pi} [\cos \alpha + \cos \alpha]$$

$$V_o = \frac{2V_m \cos \alpha}{\pi}$$

Q. RMS & O.P. Voltage (VRMS) :-

$$V_{RMS} = \sqrt{\frac{1}{\pi} \int_{-\pi}^{\pi} V_{in}^2 d\theta} \quad \text{but } V_{in} = V_m \sin \theta$$

$$V_{RMS} = \sqrt{\frac{1}{\pi} \int_{-\pi}^{\pi} (V_m \sin \theta)^2 d\theta} = \sqrt{\frac{V_m^2}{\pi} \int_{-\pi}^{\pi} \sin^2 \theta d\theta}$$

$$V_{RMS} = \sqrt{\frac{V_m^2}{\pi} \int_{-\pi}^{\pi} \left(\frac{1 - \cos 2\theta}{2} \right) d\theta} = \sqrt{\frac{V_m^2}{2\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_{-\pi}^{\pi}}$$

$$V_{RMS} = \sqrt{\frac{V_m^2}{2\pi} \left[(\pi + \alpha) - \alpha - \frac{\sin 2(\pi + \alpha)}{2} + \frac{\sin 2\alpha}{2} \right]}$$

$$V_{RMS} = \sqrt{\frac{V_m^2}{2\pi} \left[\pi - \frac{\sin(2\pi + 2\alpha)}{2} + \frac{\sin 2\alpha}{2} \right]}$$

but $\sin(2\pi + \phi) = \sin \phi$

$$\therefore V_{RMS} = \sqrt{\frac{V_m^2}{2\pi} \left[\pi + \left(-\frac{\sin(2\pi)}{2} + \frac{\sin 2\alpha}{2} \right) \right]}$$


$$V_{RMS} = \sqrt{\frac{V_m^2}{2\pi}} \cdot \cancel{\pi}$$

$$\boxed{V_{RMS} = \frac{V_m}{\sqrt{2}}}$$



08/02/24

Lecture 5 :- Semiconductor

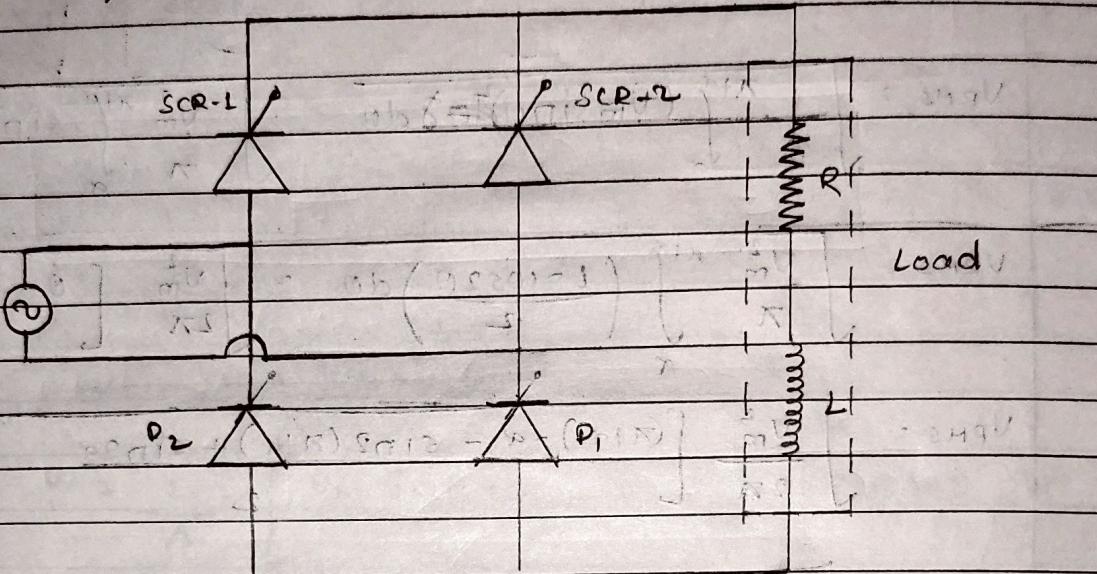* ~~Half controlled converter (semiconductor) in single Phase full wave half controlled bridge converter :-~~



Pulse + (Symmetrical)

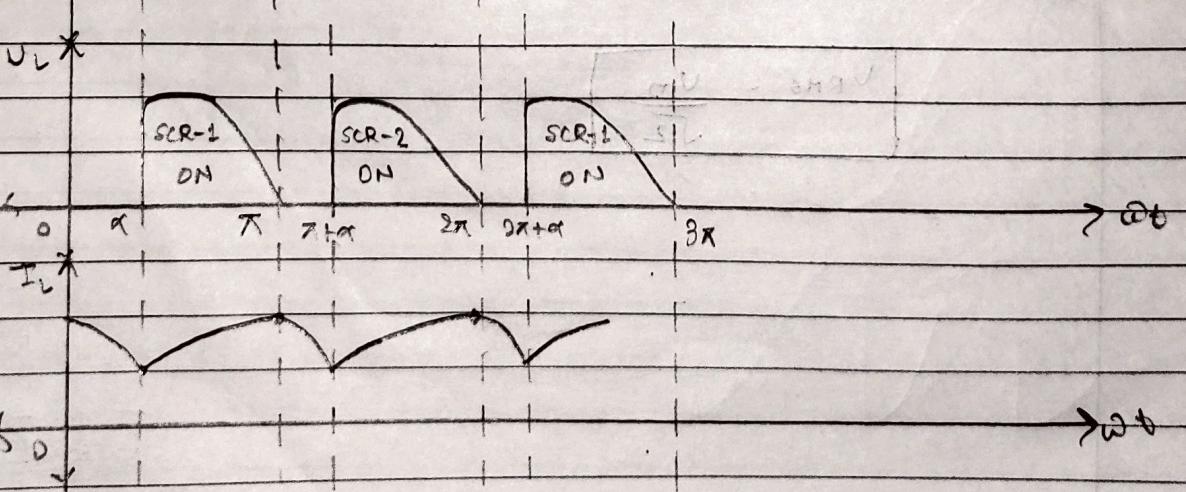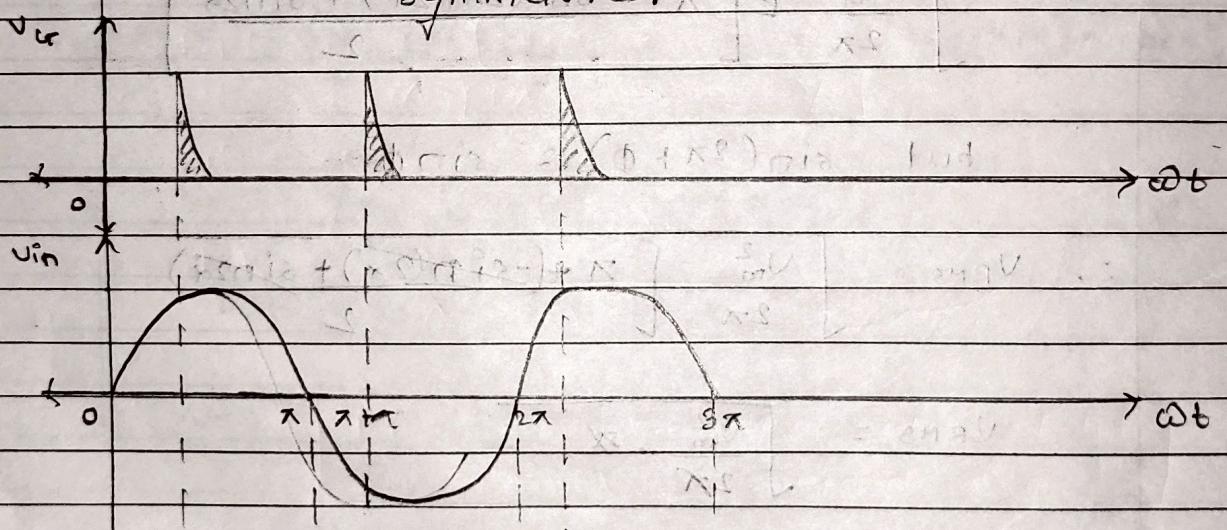

Operation:-

Mode

Mode	I $(\alpha - \pi)$	II $(\pi - (\pi + \alpha))$	III $(\pi + \alpha) - 2\pi$	IV $[0 - \alpha]$
Conducting device	SCR1 - D1	DFW	S2 D2	DFW
Load voltage	Positive	Zero	Positive	zero
Load current	Positive	Positive	Positive	Positive
Power flow	Source to Load	Free-wheeling	Source to Load	Free-wheeling

Performance analysis:-

1. Average output voltage (V_o) :-

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\pi} v_{in} d\theta$$

$$\text{but } v_{in} = V_m \sin \theta$$

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \theta d\theta = \frac{V_m}{\pi} [\pm \cos \theta]_{\alpha}^{\pi}$$

$$V_o = \frac{V_m}{\pi} [\cos(\alpha) - \cos(\pi)]$$

$$V_o = \frac{V_m}{\pi} [1 + \cos(\alpha)]$$

2. RMS voltage (V_{rms}) :-

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} v_{in}^2 d\theta} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \theta d\theta}$$

$$V_{rms} = \sqrt{\frac{V_m^2}{\pi} \int_{\alpha}^{\pi} (1 - \cos 2\theta) d\theta}$$

$$V_{RMS} = \sqrt{\frac{V_m^2}{2\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^\pi}$$

$$V_{RMS} = \sqrt{\frac{V_m^2}{2\pi} \left\{ (\pi - \alpha) - \left[\frac{\sin(2\pi) - \sin(2\alpha)}{2} \right] \right\}}$$

$$V_{RMS} = \frac{V_m}{\sqrt{2\pi}} \sqrt{(\pi - \alpha) + \frac{\sin(2\alpha)}{2}}$$

3. Power factor (P.F) :-

$$P.F = \frac{V_o^2}{V_{RMS}^2} = \frac{V_m^2}{\pi^2} (1 + \cos \alpha)^2$$

$$= \frac{V_m^2}{\pi^2} \left\{ (\pi - \alpha) + \frac{\sin(2\alpha)}{2} \right\}^2$$

$$P.F = \frac{2}{\pi} \frac{[1 + \cos(\alpha)]^2}{[(\pi - \alpha) + \sin(2\alpha)/2]}$$



if $\alpha = 0$

$$P.F = \frac{2}{\pi}, \frac{4}{\pi}$$

$$P.F = \frac{8}{\pi^2} \quad [\text{Max. value of P.F provided } \alpha = 0]$$

19/02/24 Lecture 6 :-

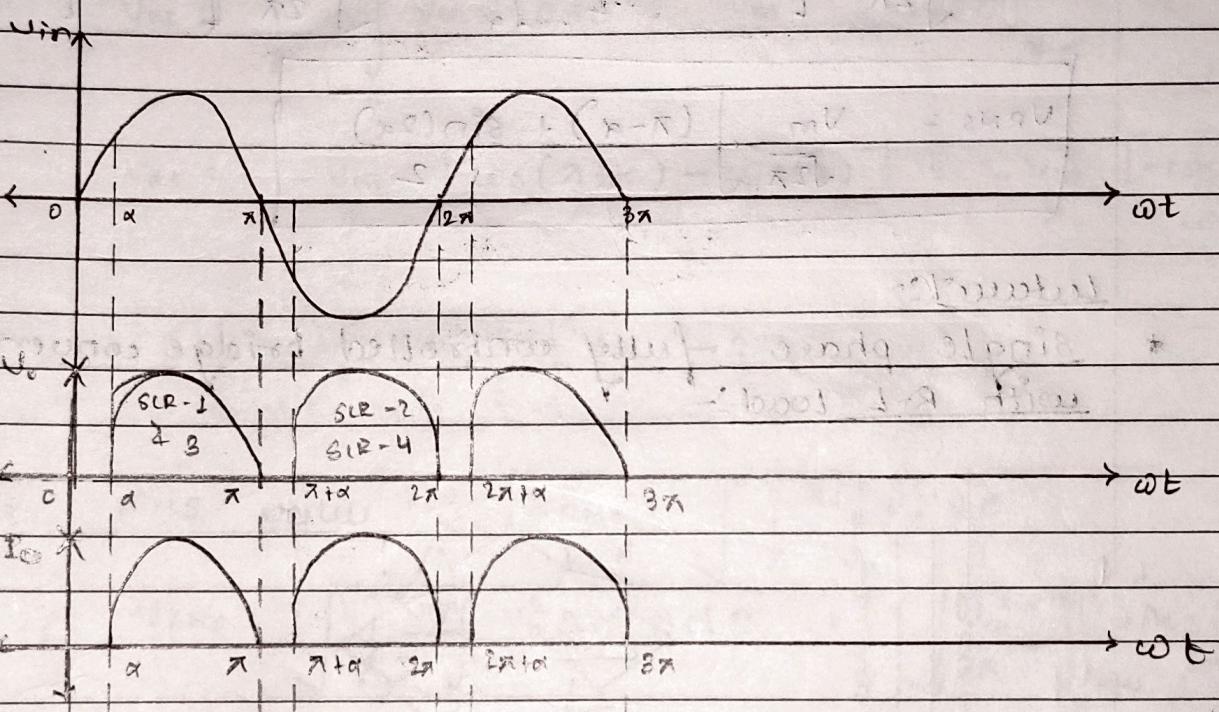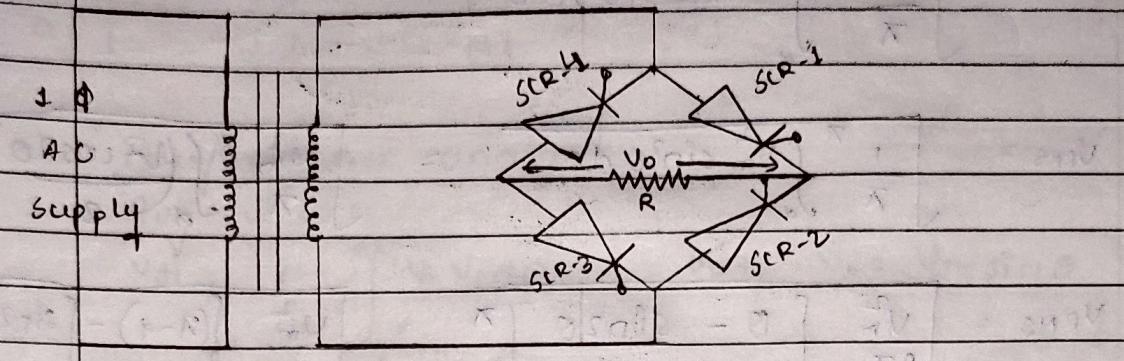* Single phase fully controlled rectifier for A-Load (Bridge converter) :-



Performance analysis:-

1. Average OLP :-

$$V_{avg} = V_{dc} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \theta d\theta = \frac{V_m}{\pi} [-\cos \theta]_{\alpha}^{\pi}$$

$$V_{dc} = -\frac{4V_m}{\pi} [\cos(\pi) + \cos(\alpha)]$$

$$V_{dc} = \frac{V_m}{\pi} [1 + \cos(\alpha)]$$

2. RMS of p.voltage :- $V_{RMS} = \sqrt{\frac{1}{\pi} \int_0^{\pi} V_o^2 d\theta}$

$$V_{RMS} = \sqrt{\frac{1}{\pi} \int_0^{\pi} (V_m \sin \theta)^2 d\theta}$$




$$V_{RMS} = \sqrt{\frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2 \theta d\theta} = \sqrt{\frac{V_m^2}{\pi} \int_0^{\pi} \frac{(1 - \cos 2\theta)}{2} d\theta}$$


$$V_{RMS} = \sqrt{\frac{V_m^2}{2\pi}} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^{\pi} = \sqrt{\frac{V_m^2}{2\pi}} \left[(\pi - \alpha) - \frac{\sin 2\pi - \sin 2\alpha}{2} \right]$$

$$V_{RMS} = \frac{V_m}{\sqrt{2\pi}} \int_0^{\pi} \frac{(\pi - \alpha) + \sin(2\alpha)}{2} d\theta$$

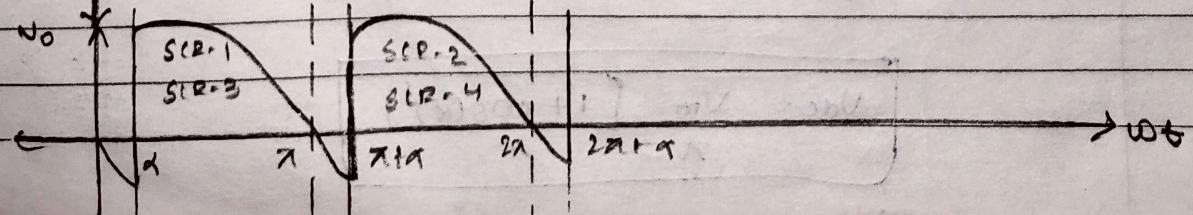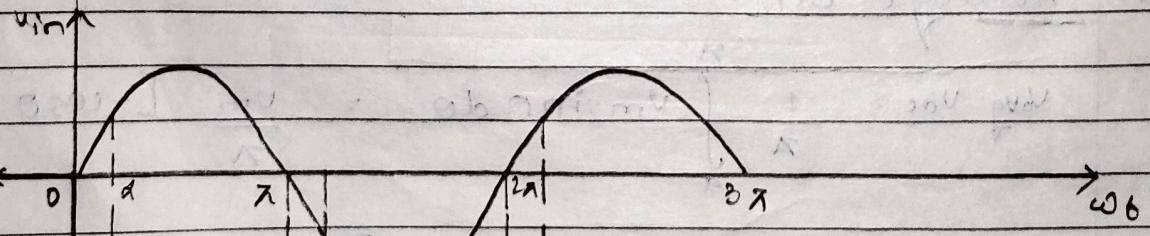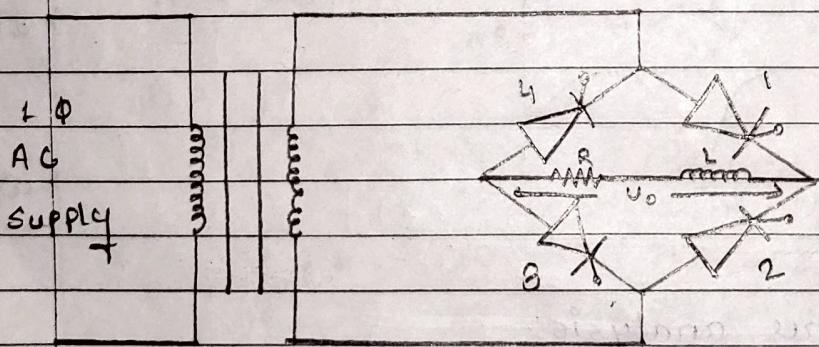QUESTION :-

* single phase fully controlled bridge converter with R-L load :-



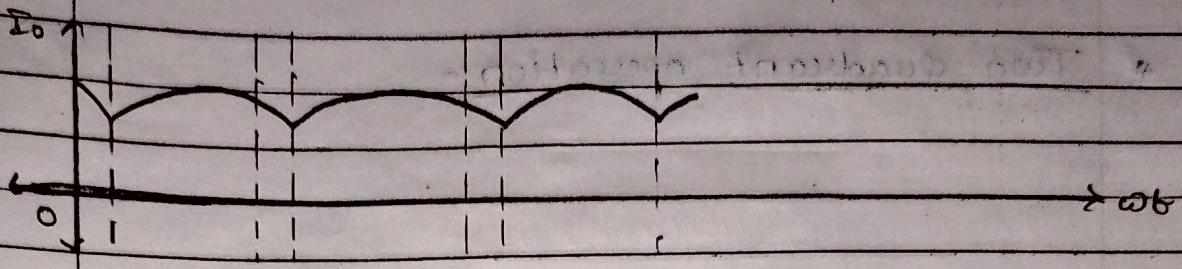

Performance analysis:-

1. Avg. value :-

$$V_{dc} = \frac{1}{\pi} \int_{-\pi}^{\pi} V_o d\theta \quad \text{but } V_o = V_m \sin \theta$$

$$V_{dc} = \frac{1}{\pi} \int_{-\pi}^{\pi} V_m \sin \theta d\theta = \frac{V_m}{\pi} [-\cos \theta]_{-\pi}^{\pi}$$

$$V_{dc} = -\frac{V_m}{\pi} [\cos(\pi + \alpha) - \cos(\alpha)] = -\frac{V_m}{\pi} [-\cos \alpha - \cos \alpha]$$

$$\boxed{V_{dc} = \frac{2V_m}{\pi}} \quad \boxed{V_{dc} = \frac{2V_m \cos(\alpha)}{\pi}}$$

$$2. \text{ RMS value} := V_{RMS} = \sqrt{\frac{1}{\pi} \int_{-\pi}^{\pi} V_o^2 d\theta}$$

$$V_{RMS} = \sqrt{\frac{1}{\pi} \int_{-\pi}^{\pi} V_m^2 \sin^2 \theta d\theta} = \sqrt{\frac{V_m^2}{\pi} \int_{-\pi}^{\pi} \frac{1 - \cos(2\theta)}{2} d\theta}$$

$$V_{RMS} = \sqrt{\frac{V_m^2}{2\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_{-\pi}^{\pi}}$$

$$V_{RMS} = \frac{V_m}{\sqrt{2\pi}} \sqrt{(2\pi + \alpha - \alpha) - \left\{ \sin(2\pi + 2\alpha) - \sin(2\alpha) \right\}} = \frac{V_m}{\sqrt{2\pi}} \sqrt{2\pi}$$

$$V_{RMS} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\pi - \left\{ \sin(2\alpha) - \sin(2\alpha) \right\}} = \frac{V_m}{\sqrt{2\pi}} \sqrt{2\pi}$$

$$\boxed{V_{RMS} = \frac{V_m}{\sqrt{2}}}$$

Lecture 8 :-

* Solved Problems of Semiconductor (Half) :-

i) $V_{IRMS} = \frac{V_m}{\sqrt{2}}$ ii) $V_{OAV} = \frac{V_m}{\pi} [1 + \cos(\alpha)]$

iii) $V_{ORMS} = \sqrt{\frac{V_m^2}{2\pi}} \left[(\pi - \alpha) + \frac{\sin(2\alpha)}{2} \right]$

iv) D.F = $\cos\left(\frac{-\alpha}{2}\right)$ v) $I_{SRMS} = I_0 \sqrt{\frac{(\pi - \alpha)}{\pi}}$

vi) $I_{SRMS} = \frac{2\sqrt{2} I_0}{\pi} \cos\left(\frac{\pi\alpha}{2}\right)$ vii) Radian = $\frac{\pi}{180}$ rdegree

- Q:- A single phase semiconductor with highly inductive load is feed from 120V AC mains & fired at $\alpha = 90^\circ$. calculate i) Average load voltage ii) RMS load voltage iii) Displacement factor.

→ $V_{IRMS} = 120V$, $\alpha = 90^\circ$

$V_{IRMS} = \frac{V_m}{\sqrt{2}}$ ∴ $V_m = 120\sqrt{2}$

$V_{OAV} = \frac{V_m}{\pi} (1 + \cos\alpha) = \frac{120\sqrt{2}}{\pi} (1 + \cos 90^\circ)$

$V_{OAV} = 54.0189V$

$V_{ORMS} = \sqrt{\frac{V_m^2}{2\pi}} \left[(\pi - \alpha) + \frac{\sin(2\alpha)}{2} \right]$

$\alpha = 90^\circ \Rightarrow \text{Radian} = \frac{\pi}{2} \times \frac{90}{180} = \frac{\pi}{2}$

$$V_{\text{RMS}} = \sqrt{\frac{(120\sqrt{2})^2}{2\pi} \left\{ \left(1 - \frac{\pi}{2}\right) + \frac{\sin(2\pi 90)}{2} \right\}}$$

$$V_{\text{RMS}} = \sqrt{\frac{14400\pi^2}{2\pi} \times \frac{\pi}{2}}$$

$$V_{\text{RMS}} = 84.8528 \text{ V}$$

$$\text{D.F.} = \cos\left(\frac{\alpha}{2}\right) = \cos\left(-90^\circ\right)$$

$$[\text{D.F.} = 0.7071]$$

Q:2 A single phase half controlled bridge rectifier supplies a ripple-free load current of 10A & operates from 110V, 60Hz mains. If average o/p voltage is 75V. Calculate.

- i) Firing angle ii) RMS o/p voltage iii) RMS supply current iv) RMS 3rd harmonic supply current.

$$\rightarrow I_o = 10 \text{ A}, V_{\text{RMS}} = 110 \text{ V}, V_{\text{AV}} = 75 \text{ V}$$

$$i) \alpha = ?$$

$$V_{\text{RMS}} = V_m \Rightarrow V_{\text{RMS}} = \frac{110\sqrt{2}}{\sqrt{2}}$$

$$V_{\text{AV}} = \frac{V_m}{\pi} (1 + \cos\alpha) \Rightarrow 75 = \frac{110\sqrt{2}}{\pi} [1 + \cos(\alpha)]$$

$$1 + \cos(\alpha) = \frac{75\pi}{110\sqrt{2}} \Rightarrow \cos(\alpha) = \frac{75\pi}{110\sqrt{2}}$$

$$\alpha = \cos^{-1}\left(\frac{75\pi}{110\sqrt{2}}\right)$$

$$\alpha = 59.8259^\circ = 59.8259\pi \text{ rad}$$

$$\alpha = 1.0302 \text{ rad}$$

$$V_{ORMS} = \frac{110\sqrt{2}}{2\pi} \left\{ (\frac{-0.30\pi - 0.10302}{2}) + \sin(2\pi 39.02) \right\}$$

$$[V_{ORMS} = 99.1557 \text{ V}]$$

$$I_{SPMS} = I_0 \sqrt{\frac{(\pi - \alpha)}{\pi}} = 10 \sqrt{\frac{(\pi - 1.0302)}{\pi}}$$

$$[I_{SPMS} = 8.1980 \text{ A}]$$

$$I_{ORMS} = \frac{2\sqrt{2}}{\pi} I_0 \cos\left(\frac{\pi\alpha}{2}\right) = \frac{2\sqrt{2} \times 10 \cos(39.02)}{8\pi}$$

Lecture 9:- Full converter using SCR (Solved Problems)

$$1. V_m = \sqrt{2} V_{IRMS} \quad 2. V_{OAV} = \frac{V_m}{\pi} [1 + \cos(\alpha)]$$

$$3. V_{ORMS} = \frac{V_m}{\sqrt{2\pi}} \left[(\pi - \alpha) + \frac{\sin(2\alpha)}{2} \right]$$

$$4. P_{OACV} = \frac{V_{OAV}}{R} \quad 5. I_{OCRMS} = \frac{V_{OCRMS}}{R}$$

$$6. F.F = \frac{V_{OCRMS}}{V_{OAV}} \quad 7. R.F = \sqrt{F.F^2 - 1}$$

Ques: A $\pm \Phi$ full controlled converter with resistive load ($R = 10\Omega$) & i/p voltage 230V. Calculate for $\alpha = 60^\circ$

- i) Average load voltage ii) RMS load voltage
- iii) Average & RMS load current.
- iv) Form factor & Ripple factor.

$$R = 10\Omega \quad V_{rms} = 230V, \quad \alpha = 60^\circ = \frac{\pi}{3}$$

$$\sqrt{2}V_{rms} = \sqrt{2}V_m \quad V_m = 230\sqrt{2}$$

i) $\underline{V_{av}} = V_{av} = \frac{V_m}{\pi} [1 + \cos(\alpha)] = \frac{230\sqrt{2}}{\pi} \left[1 + \frac{1}{2} \cos\left(\frac{\pi}{3}\right) \right]$

$$V_{av} = \frac{230\sqrt{2}}{\pi} \quad \boxed{V_{av} = 155.3045V}$$

ii) $V_{rms} = \sqrt{\frac{V_m^2}{2}}$

ii) $V_{rms} = \frac{V_m}{\sqrt{2\pi}} \cdot \sqrt{(\pi - \alpha) + \frac{\sin(2\alpha)}{2}}$

$$V_{rms} = \frac{230\sqrt{2}}{\sqrt{2\pi}} \cdot \sqrt{\left(\pi - \frac{\pi}{3}\right) + \frac{\sin(120^\circ)}{2} + \frac{\sin(240^\circ)}{2}}$$

$$\boxed{V_{rms} = 206.2958V}$$

iii) $I_{av} = \frac{V_{av}}{R} = \frac{155.3045}{10} = 15.53A$

$$I_{rms} = \frac{V_{rms}}{R} = \frac{206.2958}{10} = 20.62A$$

iv) $F.F = \frac{V_{rms}}{V_{av}} = \frac{206.2958}{155.3045} = 1.3283$

$$R.F = \sqrt{(F.F)^2 - 1} = \sqrt{0.8748}$$

$P.F = \cos(\alpha) = \cos(60^\circ) = \frac{1}{2}$
Power factor

$$V_m = \sqrt{2} V_{IRMS}, \quad V_{OAV} = \frac{2V_m \cos \alpha}{\pi} \quad P.F \{ \text{Fundamental} \}$$

$$= \cos(-\alpha)$$

$$P.F \{ \text{SUPPLY} \} = \frac{2\sqrt{2}}{\pi} \cos(\alpha)$$

- Q22 A single phase fully controlled bridge converter supplies an inductive load. Assume I_0 is constant.
- Determine the following if $V_{IN} = 230V$, $\alpha = 30^\circ$
- Average output voltage
 - Fundamental P.F
 - Supply P.F

~~$$V_{IRMS} = 230V, \quad \alpha = \frac{\pi}{6} = 30^\circ$$~~

~~$$V_{IRMS} = \frac{V_m}{\sqrt{2}} \Rightarrow V_m = 230\sqrt{2} V$$~~

~~$$i) V_{OAV} = \frac{V_m [1 + \cos(4\alpha)]}{\pi} = \frac{230\sqrt{2}}{\pi} \left[1 + \cos\left(\frac{\pi}{3}\right) \right]$$~~

$$V_{OAV} = 193.2015 V$$

~~$$V_{IRMS} = 230V, \quad \alpha = \frac{\pi}{6} = 30^\circ \quad V_m = \sqrt{2} V_{IRMS}$$~~

~~$$\therefore V_m = 230\sqrt{2} V$$~~

~~$$ii) V_{OAV} = \frac{2V_m \cos(\alpha)}{\pi} = \frac{2 \times 230\sqrt{2}}{\pi} \cos(30^\circ)$$~~

$$V_{OAV} = 179.33 V$$

~~$$iii) P.F = \cos(-\alpha) = \cos(-30^\circ) = 0.8668 \quad (\text{lagging})$$~~

~~$$iv) P.F = \frac{2\sqrt{2} \cos(30^\circ)}{\pi} = 0.78 \quad (\text{lagging})$$~~

Q.8 A 3Ø full converter from 3Ø star connected 208 V, 60 Hz supply with 'R' load of 10Ω . It is required to obtain 80% of max. possible output voltage. ~~to calculate~~ i) Delay angle ii) RMS & avg. currents.

\Rightarrow $V_{LRMS} = 208\text{V}$

$$R = 10 \Omega$$

\Rightarrow 80

$$1. V_m(\text{line}) = \sqrt{3} \times \sqrt{2} V_m(\text{ph}) \quad 2. V_{LDC(\text{max})} = \frac{3 V_m(\text{line})}{\pi}$$

$$3. V_{LDC} = \frac{3 V_m(\text{line}) \cos(\alpha)}{\pi} \quad 4. I_{LDC} = \frac{V_{LDC}}{R_L} \quad 5. I_{LRMS} = \frac{V_{LRMS}}{R}$$

$$\therefore V_{LRMS} = V_m(\text{line}) \cdot \sqrt{\frac{1}{2} + \frac{3\sqrt{3}}{4\pi} \cos(2\alpha)}$$

$$\Rightarrow V_m(\text{ph}) = 208\text{V}$$

$$V_m(\text{line}) = \sqrt{3} \times \sqrt{2} \times 208 \Rightarrow V_m(\text{line}) = 208\sqrt{6}$$

$$V_m(\text{line}) = 509.4938\text{V}$$

$$\therefore V_{LDC(\text{max})} = \frac{3 V_m(\text{line})}{\pi} = \frac{3 \times 509.4938}{\pi}$$

$$V_{LDC(\text{max})} = 486.53\text{V}$$

$$50\% \text{ of } V_{LDC(\text{max})} = \frac{50}{100} \times 486.53 \\ = 243.26\text{V}$$

$$243.26 : \frac{3 \times 509.49 \cos(\alpha)}{\pi} \Rightarrow \cos(\alpha) = \frac{243.26}{3 \times 509.49}$$

$$\alpha = 60^\circ$$

$$2. I_{LDC} = \frac{V_{LDC}}{R} = \frac{243.26}{10} \Rightarrow I_{LDC} = 24.326\text{A}$$

Q. $I_{CRMS} = \frac{V_{LRMS}}{R}$

$$V_{LRMS} = 509.49, R = 1 + \sqrt{3} \text{ (at } 60^\circ)$$


$$I_{CRMS} = 275.9028 \text{ A}$$

$$I_{CRMS} = 275.9028$$

$$I_{CRMS} = 27.59 \text{ A}$$

25/02/24 Lecture 10:-

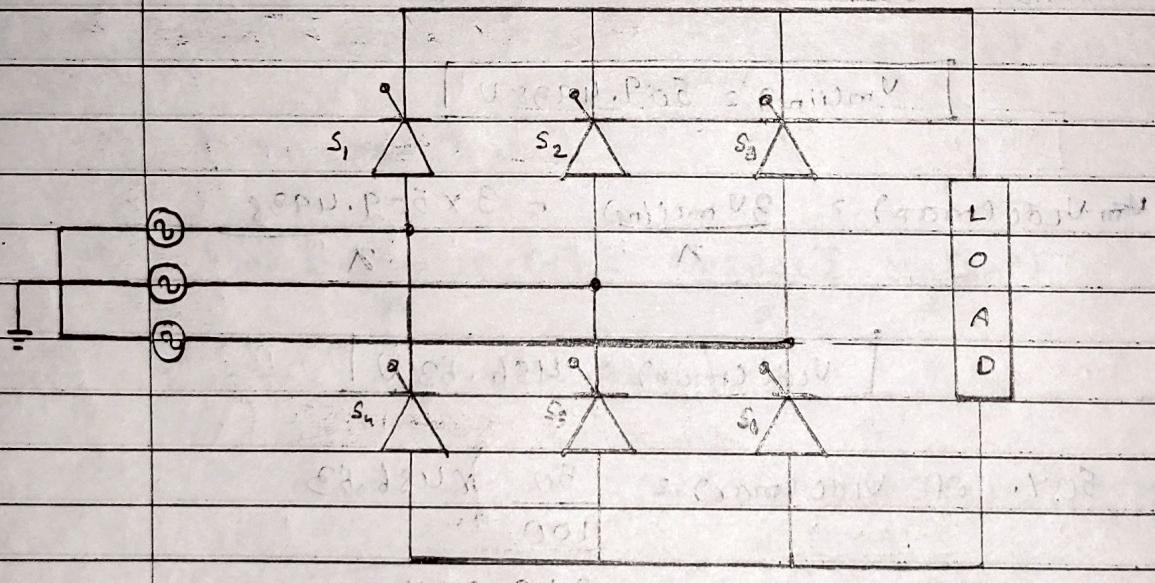* Three Phase Full converter using SCR with R-load:-



Interval	I	II	III	IV	V	VI
conducting pair	1,5	1,6	2,6	2,4	3,4	3,5
Load Voltage	V_{RY}	V_{RB}	V_{YB}	V_{YR}	V_{BR}	V_{BY}

1. In 0°-60°-120° - Δ . C.R.S. & 30°-60°-90° .
 $\Rightarrow R - Y - B$)

Just for understanding

Steps for drawing waveform:-

1. Mark 5 horizontal lines.
2. Mark L, M, N on Line-2 (Phase cross-over points on +ve side)
3. Place points on centre of these points on Line-1.
(Peak voltage points on +ve side).
4. Mark same points on Line 4 (O, P, Q)
5. Place points at centre of O, P, Q on Line 3 (Peak voltage points on -ve side)
6. Join the points using sine wave.

Waveforms:-

